



UNIT 1

Syllabus **Semiconductor Diode:** Depletion layer, V-I characteristics, ideal and practical Diodes, Diode Equivalent Circuits, Zener Diodes breakdown mechanism (Zener and avalanche) **Diode Application:** Diode Configuration, Half and Full Wave rectification, Clippers, Clampers, Zener diode as shunt regulator, Voltage-Multiplier Circuits
Special Purpose two terminal Devices: Light-Emitting Diodes, Photo Diodes, Varactor Diodes, Tunnel Diodes.



DATE / /
PAGE NO. 1

Unit Ist

Classification Of Materials

according to Conductivity

- ① Conductor: These are solids which have very low resistivity or very high conductivity
e.g. Al, Silver etc.
- ② Insulator: These are solids which have very high resistivity or very low conductivity
e.g. wood, Glass etc.
- ③ Semiconductor: These are solids which have resistivity or conductivity values between those of conductors and insulators.

Energy Band Diagram

- Energy Band: The range of energies to have an electron in a solid is known as energy band.
- Valance Band: The range of energies to have valance electrons is known as valance Band
- Conduction Band: The range of energies to have conduction electrons is known as conduction Band






DATE / /

PAGE No. 2

→ Forbidden Energy gap: The separation between conduction band and valence band on the energy level diagram is known as forbidden energy gap


Energy Band Diagram of Insulator

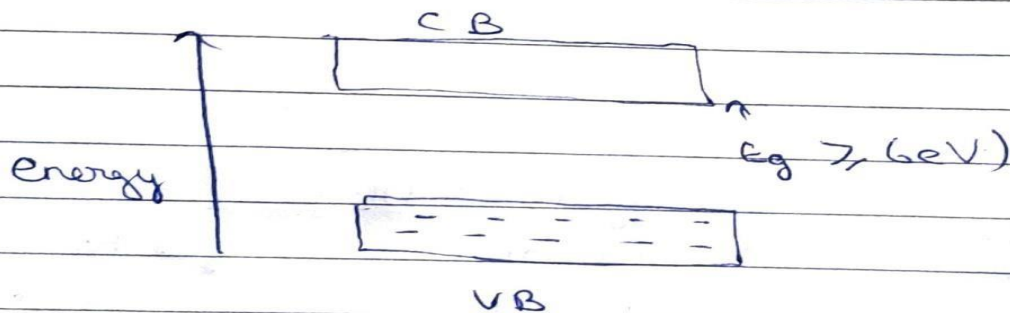In terms of energy band in insulator the valence band is full while the conduction band is empty. Further, the energy gap between valence and conduction band is very large (approx more than 6 eV). Therefore a very high electric field is required to push the valence electrons to the conduction band.



Energy Band Diagram of Conductor

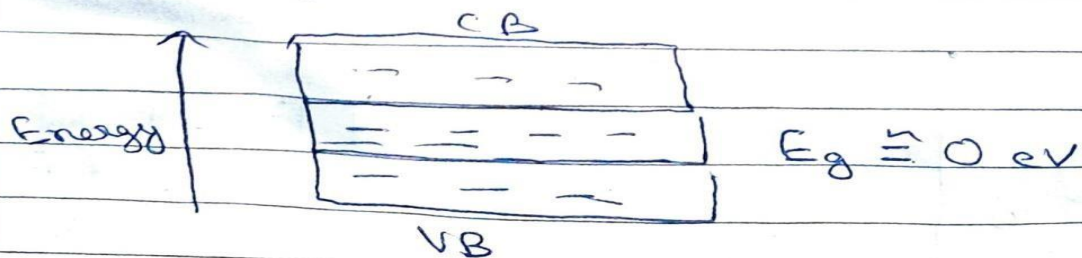In terms of energy band the valence and conduction bands overlap each other. Due to this overlapping a slight potential difference across a conductor causes the free e^- s to constitute electric current.






Date _____
Page No. 3

Energy band diagram of Semiconductor

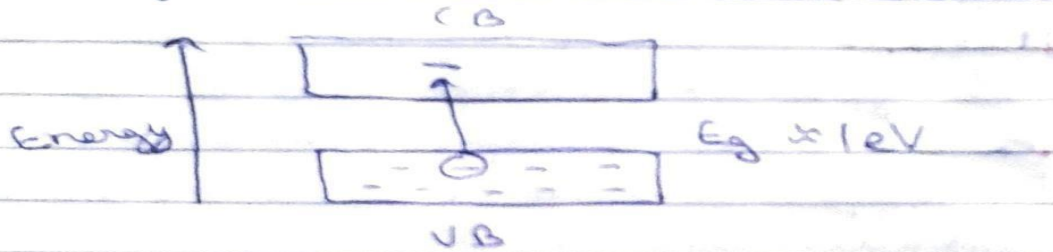
In terms of energy band, the valence band is almost filled and conduction band is almost empty. Further the energy gap between valence and conduction band is very small ($\approx 1\text{eV}$). Therefore small electric field is required to push the e^- from the valence band to the conduction band.



Note :- At low temperature the valence band is completely filled and conduction band is completely empty. Therefore a semiconductor virtually behaves as an insulator at low temperature. However at room temp some electrons cross over the conduction band imparting little conductivity to the semiconductor.

Classification of semiconductor

① Intrinsic Semiconductor

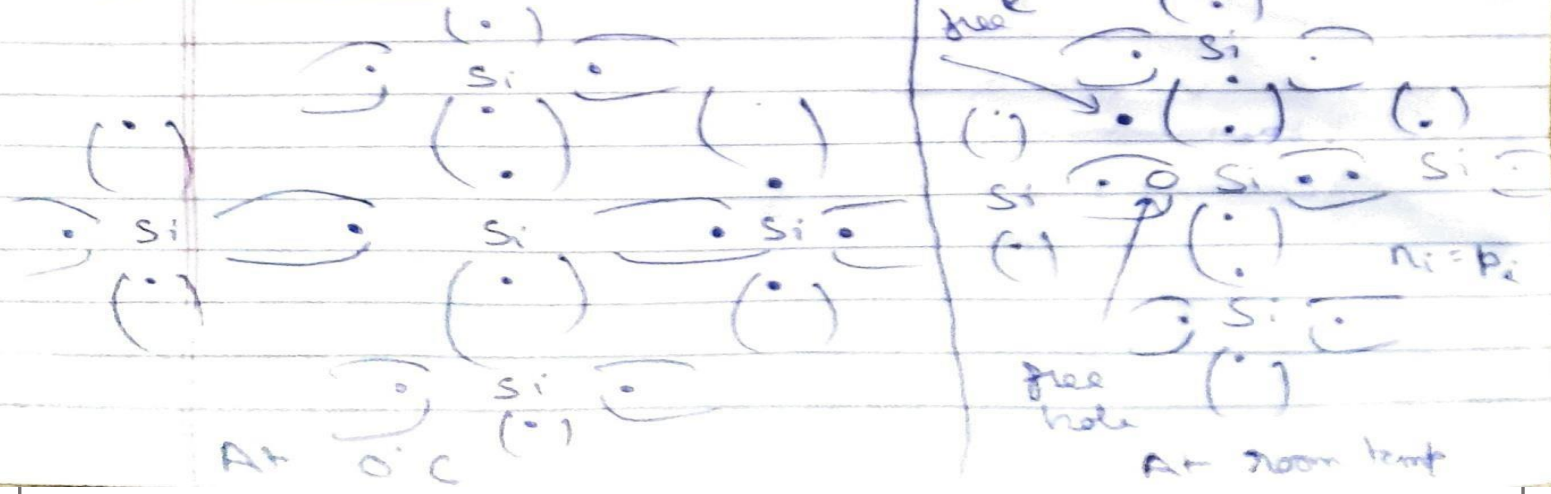



DATE / /

PAGE No. 4

A semiconductor in an extremely pure form is known as intrinsic semiconductor.

In an intrinsic semiconductor even at room temperature hole-electron pair are created. When electric field is applied across an intrinsic semiconductor, the current conduction takes place by two process mainly; by ^{free} e^- and holes. The free electrons are produced due to the breaking up of some covalent bonds by thermal energy. At the same time, holes are created in the covalent bonds. Therefore the total current inside the semiconductor is the sum of currents due to free e^- and holes.

② Extrinsic Semiconductor :-

When a small amount of impurity is added to a pure semiconductor it becomes extrinsic semiconductor.

The intrinsic semiconductor has little current conductivity at room temperature, to make it suitable for electronic applications we must change its conducting properties.

This is achieved by adding a small amount of suitable impurity to a semiconductor. The process of adding impurity to a semiconductor is known as doping.

The purpose of adding impurity is to increase either the number of free e^- or holes in the s/c crystal.

Depending upon the type of impurity added extrinsic semiconductors are classified into :-

① n type

② p type




DATE / /

PAGE No. 5

n-type Semiconductor

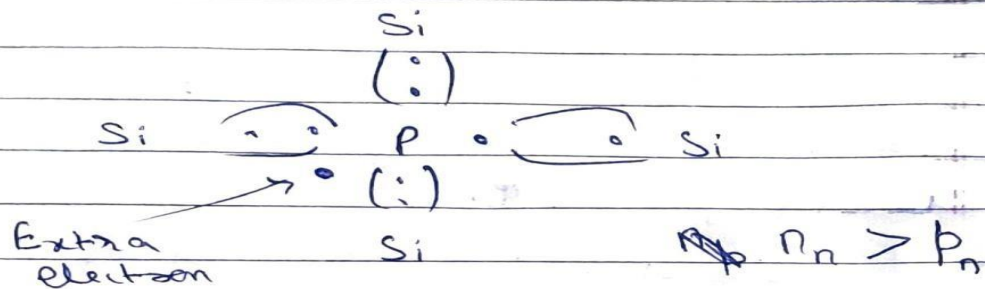
When a small amount of pentavalent impurity is added to a pure semiconductor, it is known as n-type semiconductor.



The addition of pentavalent impurity provides a large number of free electrons in the semiconductor. Pentavalent impurities are arsenic, antimony, Bismuth, Phosphorus etc. Such impurities which produce n-type semiconductor are known as donor impurities.

p-type Semiconductor

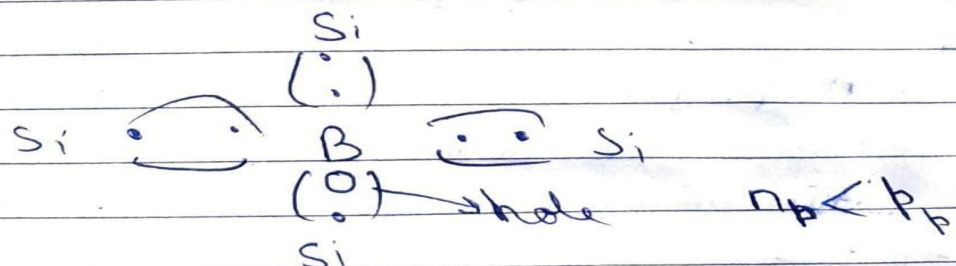
When a small amount of trivalent impurity is added to a pure semiconductor, it is called p-type s/c.




The addition of trivalent impurity provides a large number of holes in the semiconductor. Trivalent impurities are gallium, indium, boron etc. Such impurities which produce p-type s/c are known as acceptor impurities.

DATE / /
PAGE NO. 6

PN Junction diode

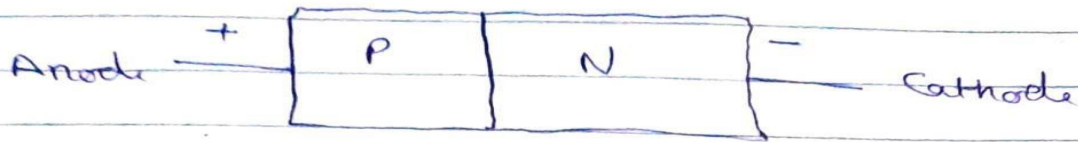

When a p-type and n-type S/C properly join together it forms pn junction. After the formation of junction a large difference in carrier density exists which results holes in the p-side tends to diffuse into n-side ^{leaving behind} ~~leaving~~ ~~in the~~ n-side trivalent ion and e⁻ in the n-side one tends to diffuse into p-side ^{leaving behind} ~~leaving~~ leaving behind pentavalent ion. Due to this charge separation a layer of -ve charge in p-type and +ve charge in n-type near the junction created. These layers of the and -ve charge form the depletion layer.

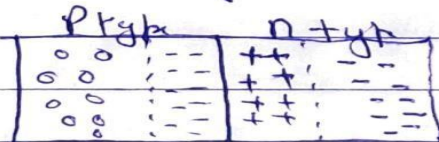

Once pn junction formed and depletion layer created the diffusion of free e⁻ stops.

Note: A pn junction is known as ~~diode~~ diode. It is a two terminal unidirectional semiconductor device. This pn junction does not allow flow of current. To make it suitable for electronics circuit, we need to biasing pn diode. These are :-

- ① Forward biasing
- ② Reverse biasing



DATE / /


PAGE No. 7

Forward biasing

In a diode when +ve voltage is applied to the n-type and +ve voltage is applied to the p-type material then the biasing is called forward biasing.

Like charges repel, so the +ve free e^- are pushed towards the pn junction. Similarly the holes are repelled by the positive terminal of the battery. If the voltage pushing the e^- and holes has sufficient strength to overcome the depletion zone the e^- and holes combine at the junction and current passes through the diode.

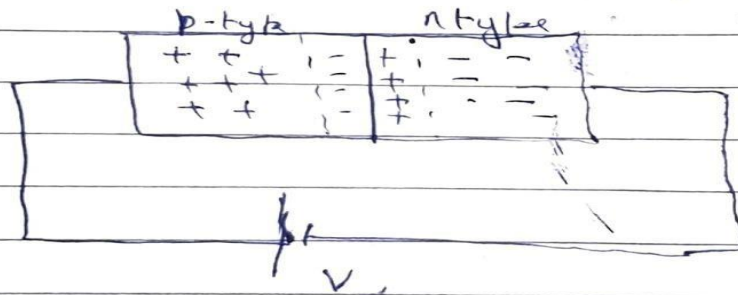The forward voltage at which the depletion region vanishes and the current in diode rises rapidly is called 'knee voltage'.



Reverse Biasing


In a diode when the voltage is applied to n-type and -ve voltage is applied to p-type material then the biasing is called Reverse Biasing.

The negative terminal attracts the +ve holes in the p-type and the +ve terminal attracts the free e^- in the n-type. All charge carriers are pulled away from pn junction which creates a larger depletion region.


But ^{there is a} small reverse leakage current because of minority carriers which is independent of reverse supply voltage called Reverse saturation current.



DATE / /
PAGE No. 9

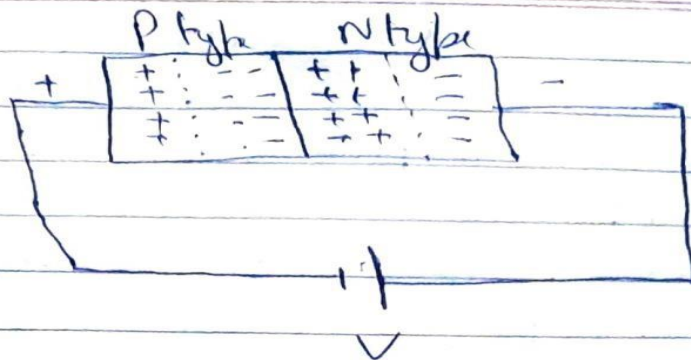

V I characteristics of pn diode

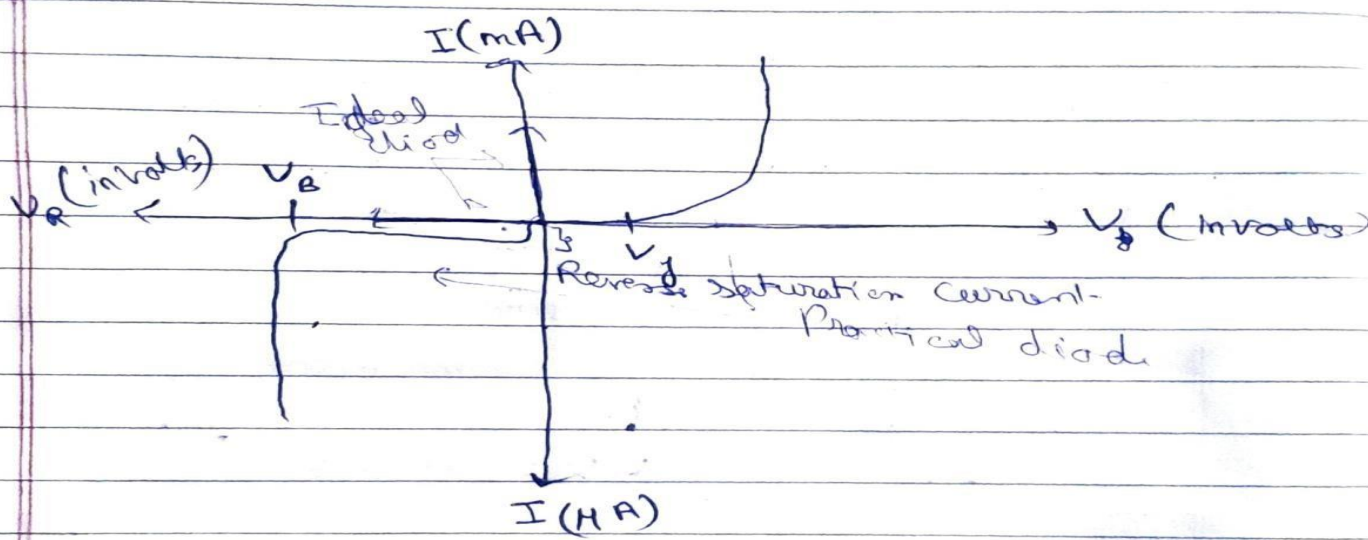

Break down in Reverse bias


- ① Zener Break down
- ② Avalanche Breakdown

Zener Break down

It occurs in highly doped diode. In highly doped diode width of depletion region is narrow. So electric field is very high in the depletion region. Due to very high electric field when reverse biased voltage increase to a certain value the heavy electric field would cause

DATE / /
Page No. 9

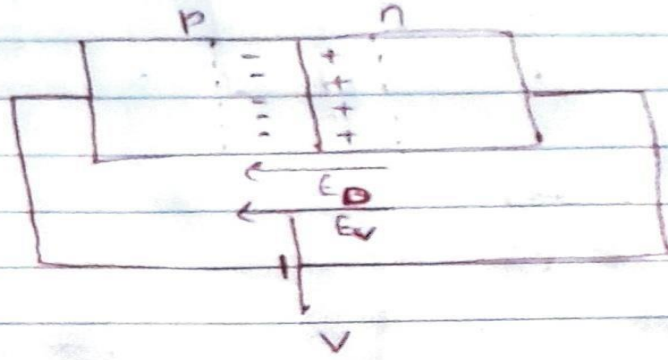
Due to these electric field ions of N-type ~~is~~ moves towards P-type. Due to these movement ~~also~~ conductivity occurs.




Avalanche Breakdown

It occurs in lightly doped diode.

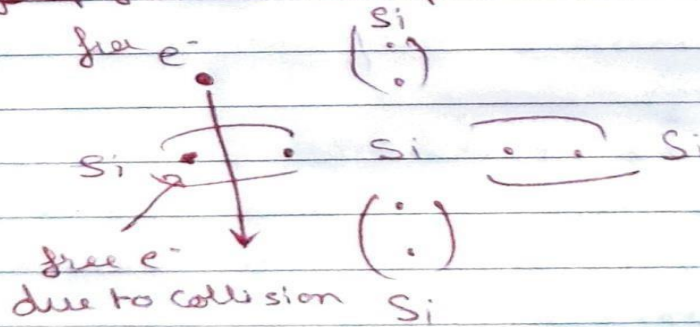
~~The process occurs when~~ When we inc. reverse voltage the kinetic energy of minority carriers inc. These accelerated minority carriers will collide with the stationary atoms and impart some of the kinetic energy to the valence e^- present. These valence e^- will break their covalent bonds and ~~form~~ free e^- -hole pair created.



Equivalent ckt of diode

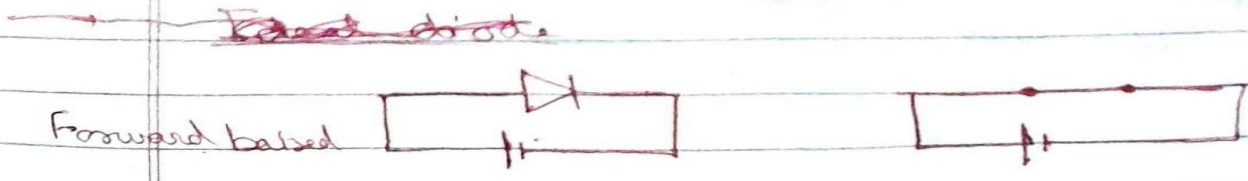


Reverse biased

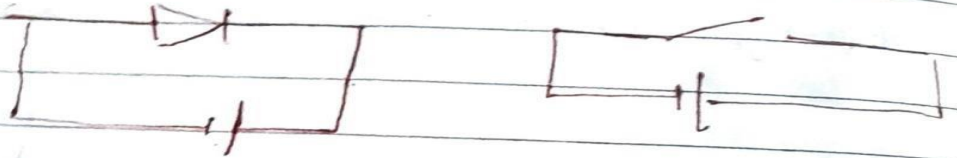

~~Practical Diode~~

~~Forward biased~~

~~Reverse biased~~

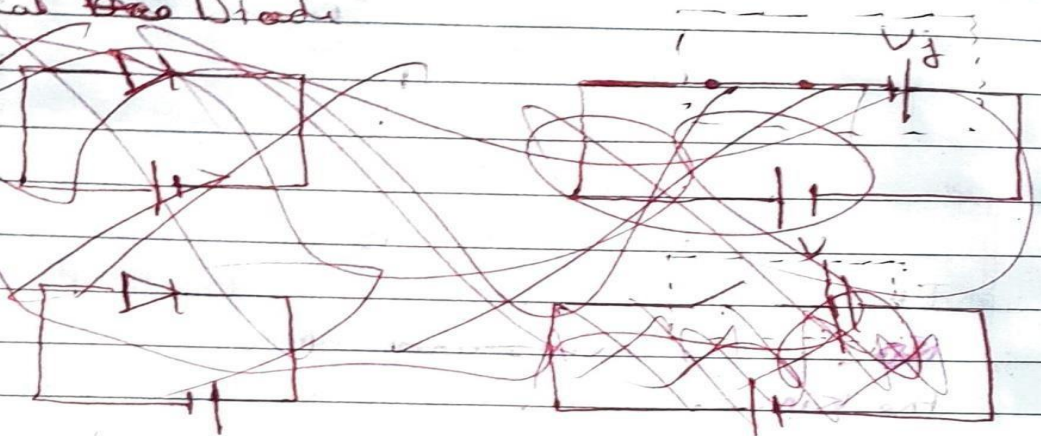


Ideal and Practical diode

In forward biased ideal diode work as a conductor where as in practical diode there is no conduction until the value of input voltage reaches the forward voltage (V_f)


In Reverse biased ideal diode work as a insulator while ~~there~~ in practical diode there is some leakage current or reverse saturation current due to minority carriers

Special Purpose Diode

① Light Emitting Diode (LED)

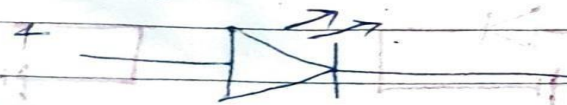

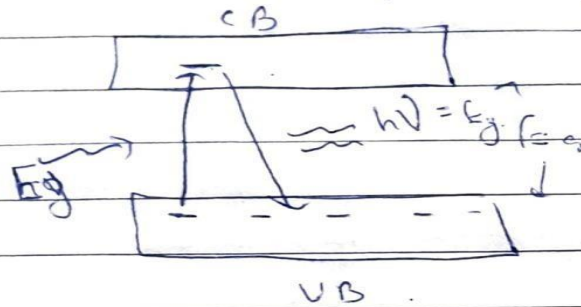It is a heavily doped PN junction diode which converts electrical energy to light energy



Energy is required to take an e^- from valence band to conduction band to generate e^- -hole pair. Conversely energy is emitted when an e^- and hole recombine.

In s/c like Si, E_g this recombination energy is emitted in the form of heat but in s/c like GaAs (Gallium Arsenide), GaP (Gallium Phosphide) the energy is emitted in the form of light. This is the basic principle of LED.


(2)

Photo Diodes




It is a device to detect and convert light energy into electrical energy. It operates in reverse bias below breakdown voltage.

$$h\nu > E_g$$

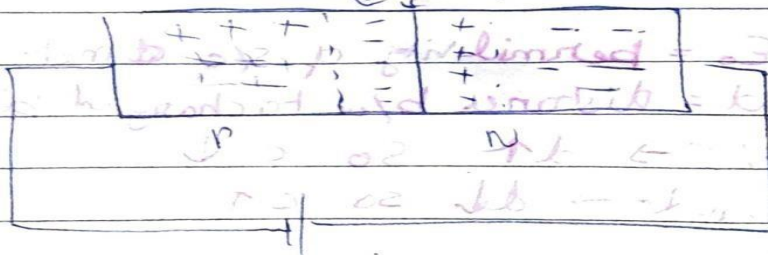


DATE / /
PAGE No. 12

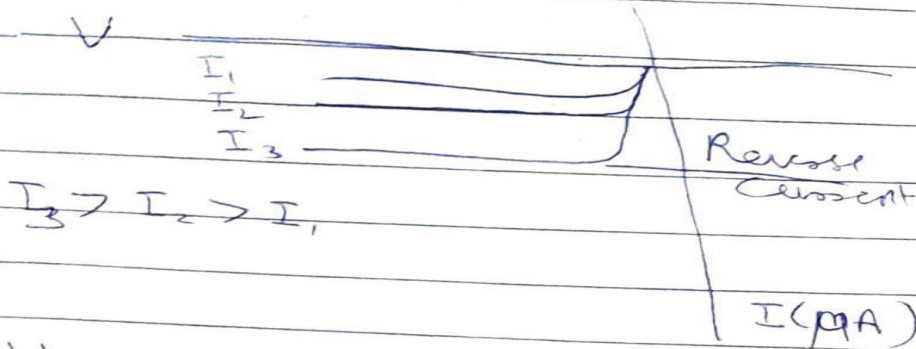When the photodiode is illuminated with light with Energy greater than E_g than e⁻ hole pairs are generated to the absorption of photons these charge carriers contribute to the reverse current



③

Varactor Diode :-

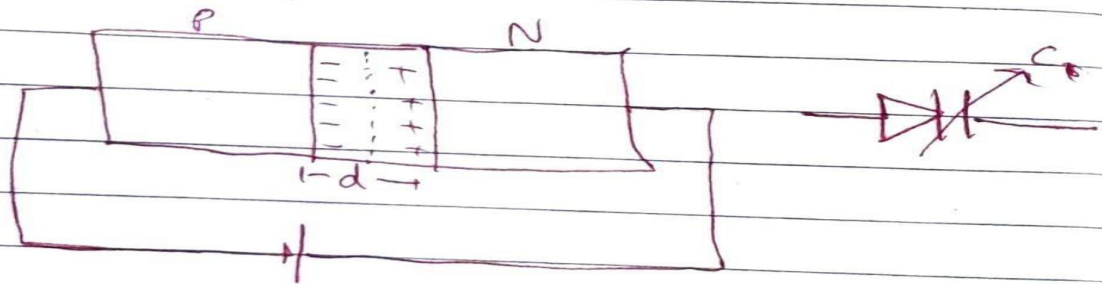

- > As voltage changes, its capacitance also changes
- > As width of depletion layer changes, its capacitance changes
- > It is always operated in reverse bias condition. Here P and N type s/c behaves like two charged plates of a capacitor and depletion layer act as dielectric

We know
$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

where ϵ_0 = permittivity of s/c material
 d = distance b/w to charged plates
 So $V \uparrow \rightarrow d \uparrow$ So $C \downarrow$
 $V \downarrow \rightarrow d \downarrow$ So $C \uparrow$

DATE / /
PAGE No. 13


(4)

Tunnel diode :-




10^3 more doping
 100 times width

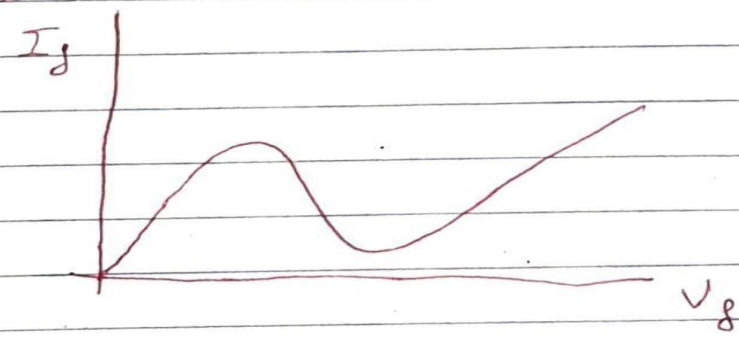P and N type s/c are highly doped so that depletion layer becomes narrow. That narrow passage is called Tunnel. When forward biasing is done then by applying a very less voltage current can start to flow as depletion layer is small so that potential barrier is less. But after a certain value they show -ve resistance between two values of forward voltage then work as a normal diode.



Rectifier

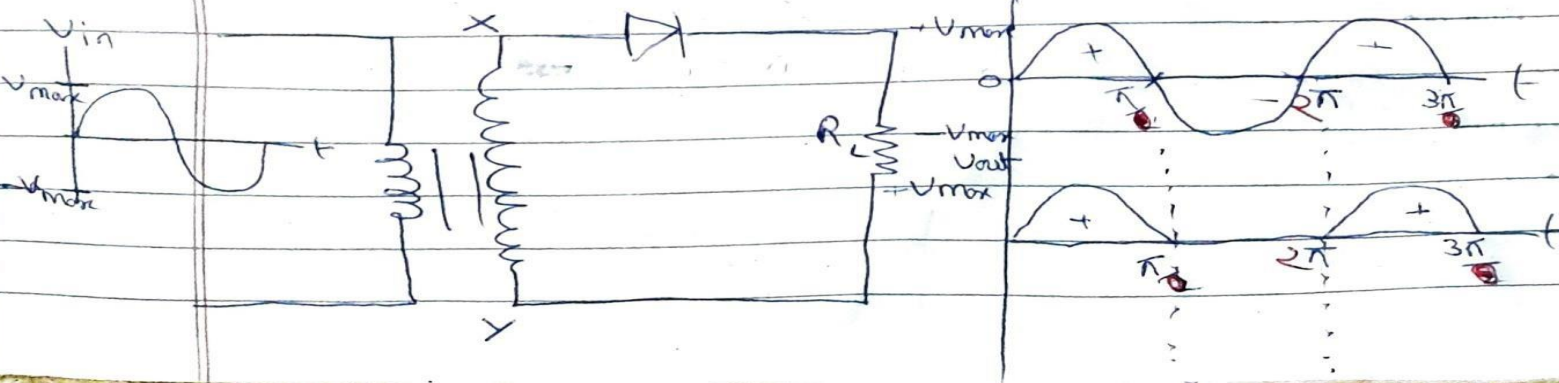- Rectifier is a ckt which convert AC to pulsated DC. There are three types of Rectifier
- (1) Half wave rectifier
 - (2) Center-tape rectifier
 - (3) Bridge rectifier





DATE / /

PAGE No. 14

During the +ve half cycle the end X of the secondary is +ve and end Y is -ve thus, forward biasing the diode (So diode act as a short ckt). As the diode is forward biased, the current flows through the load R_L and voltage is developed across it.

During the -ve half cycle the end Y is +ve and end X is -ve thus reverse biasing the diode (So diode act as a open ckt). As the diode is reverse biased, there is no flow of current through the R_L therefore the o/p voltage is 0.

I_{rms} of Half wave Rectifier

$$\begin{aligned} I_{rms} &= \sqrt{\frac{(\text{Area of one cycle of Curve})^2}{\text{Base}}} \\ &= \sqrt{\int_0^{2\pi} \frac{i^2}{2\pi} d\theta} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \theta d\theta} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{\pi} I_m^2 \sin^2 \theta d\theta + \int_{\pi}^{2\pi} 0 d\theta} \\ &= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \sin^2 \theta d\theta} \\ &= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \frac{1 - \cos 2\theta}{2} d\theta} \\ &= \sqrt{\frac{I_m^2}{4\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta} \\ &= \sqrt{\frac{I_m^2}{4\pi} \left[\theta \right]_0^{\pi} - \frac{1}{2} [\sin 2\theta]_0^{\pi}} \end{aligned}$$



DATE / /

PAGE No. 15

$$= \int \frac{I_m^2}{4\pi} (\pi - 0) - \frac{1}{2} [\sin 2\pi - \sin 0]$$

$$I_{RMS} = \frac{I_m}{2}$$

Average voltage in HWR

$$V_{average} = \frac{\text{Area under the curve}}{\text{Base}}$$

$$= \int_0^{2\pi} \frac{V_o}{2\pi} d\theta$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \theta d\theta$$

$$= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \theta d\theta + \int_{\pi}^{2\pi} 0 d\theta$$

$$= \frac{V_m}{2\pi} [-\cos \theta]_0^{\pi}$$

$$= \frac{V_m}{2\pi} [(-\cos \pi) - (-\cos 0)]$$

$$= \frac{V_m}{2\pi} [1 + 1] = \frac{V_m}{\pi}$$

$$V_{dc} = V_{average} = \frac{V_m}{\pi}$$

Ripple factor

- It measures of Purity of dc o/p of a rectifier
- The o/p voltage contains both ac and dc components so ripple factor measures the % age of ac component in the multiplier

$$\text{Ripple factor } r = \frac{\text{RMS value of AC}}{\text{Average value of DC}} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$



DATE / /

PAGE No. 16

Efficiency of HWR

$$\eta = \frac{P_{ac}}{P_{ac}} \Rightarrow P = I^2 R$$

$$P_{ac} = I_{dc}^2 R_L$$

$$P_{ac} = I_{rms}^2 R_L$$


$$\eta = \frac{I_{dc}^2 R_L}{(I_{rms})^2 R_L} = \frac{\left(\frac{I_m}{\pi}\right)^2 R_L}{\left(\frac{I_m}{2}\right)^2 R_L}$$

$$\eta = \frac{4}{\pi^2}$$

$$\eta \% = \frac{4}{\pi^2} \times 100 = 40.6 \%$$

Peak inverse voltage of HWR

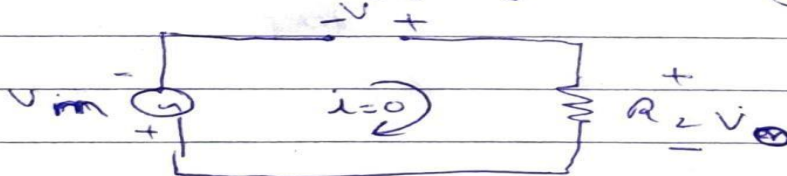Maximum Reverse bias voltage that can be applied across the diode before entering to the reverse breakd.



$$-V_m + V = 0$$

$$-V_m + V - V_o = 0$$

$$-V_m + V - i R_L = 0$$

$$-V_m + V = 0$$


$$PIV = \boxed{V = V_m}$$

Full wave Rectifier

Center tapped Rectifier :-

(1)

Center tapped rectifier

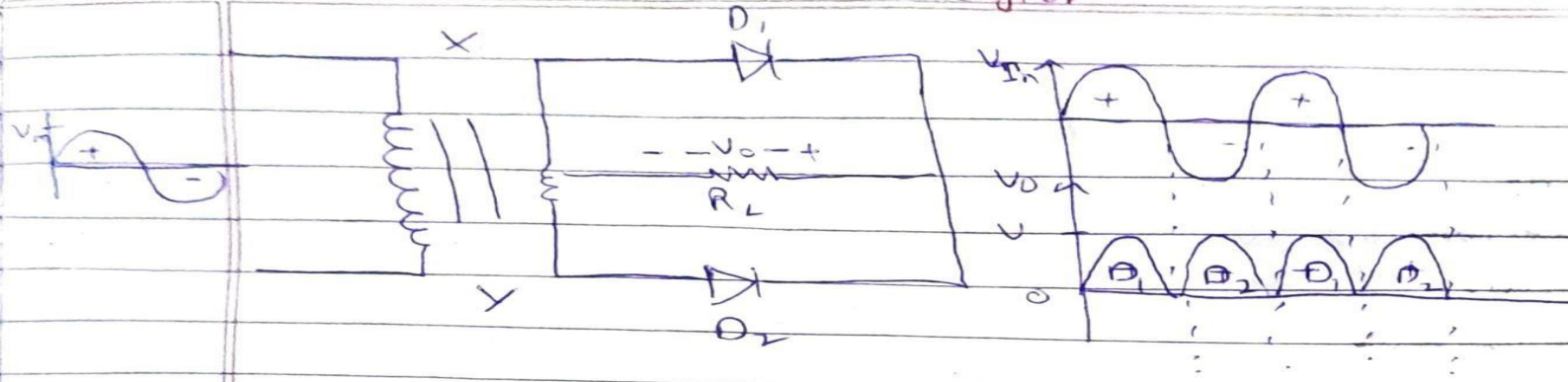

For the half cycle the end X of the secondary is +ve and end Y is -ve thus diode D_1 become forward biased and diode D_2 become Reverse biased. As the diode D_1 is forward biased the current flow through the load R_L and voltage is developed across it.

For -ve half cycle the end X of the secondary is -ve and end Y is +ve thus diode D_1 become Reverse biased and diode D_2 become forward biased. As the diode D_2 is forward biased the current flow through the load R_L and voltage is developed across it.

Irms of FWR

$$\begin{aligned}
 I_{rms} &= \sqrt{\frac{(\text{Area of one cycle of curve})^2}{\text{Base}}} \\
 &= \sqrt{\frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \theta \, d\theta} \\
 &= \sqrt{\frac{I_m^2}{\pi} \int_0^{\pi} \frac{1 - \cos 2\theta}{2} \, d\theta} \\
 &= \sqrt{\frac{I_m^2}{2\pi} \left([0]_0^{\pi} - \frac{1}{2} [\sin 2\theta]_0^{\pi} \right)} \\
 &= \sqrt{\frac{I_m^2}{2\pi} \left\{ [\pi] - \frac{1}{2} [\sin 2\pi - \sin 0] \right\}}
 \end{aligned}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$



DATE / /
PAGE No. 18

Average voltage of FWR

$$V_{avg} = \frac{\text{Area under the curve}}{\text{Base}}$$
$$= \int_0^{\pi} \frac{V_m \sin \theta}{\pi} d\theta$$
$$= \frac{V_m}{\pi} [-\cos \theta]_0^{\pi}$$

$$V_{dc} = \boxed{V_{avg} = \frac{2V_m}{\pi}}$$

Ripple factor of FWR

$$r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$
$$= \sqrt{\left(\frac{\frac{I_m}{\sqrt{2}}}{\frac{2I_m}{\pi}}\right)^2 - 1} = \sqrt{\left(\frac{\pi}{2\sqrt{2}}\right)^2 - 1}$$
$$= \sqrt{\frac{\pi^2}{8} - 1}$$
$$= 0.48$$

Efficiency of FWR


$$\eta = \frac{P_{dc}}{P_{ac}}$$
$$P_{dc} = I_{dc}^2 R_L$$
$$P_{ac} = I_{rms}^2 R_L$$
$$\eta = \frac{\left(\frac{2V_m}{\pi}\right)^2 R_L}{\left(\frac{I_m}{\sqrt{2}}\right)^2 R_L}$$
$$= \left(\frac{2\sqrt{2}}{\pi}\right)^2 = 0.81$$

$$\eta = 81\%$$



DATE / /
PAGE No. 19

Peak Inverse Voltage (PIV) (CT FWR)

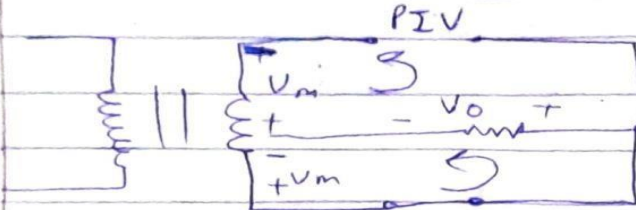

$$V_m - V_o = 0$$

$$V_o = V_m$$


Now

$$+V_o - PIV + V_m = 0$$

$$\boxed{PIV = 2V_m}$$

②

Bridge Rectifier

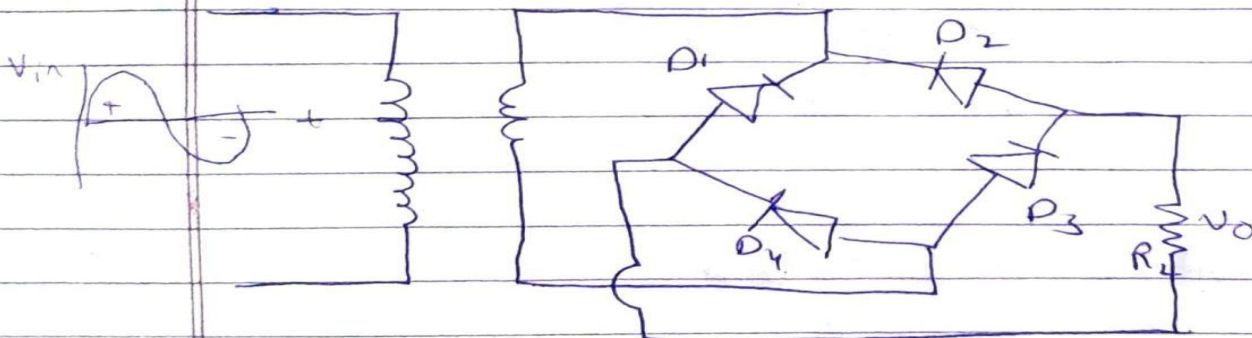

For +ve half cycle Diode D_1 and D_3 are reverse biased and diodes D_2 and D_4 are forward biased. Therefore D_2 and D_4 will conduct current across them but diodes D_1 and D_3 will not conduct. The direction of current shown. Due to current through R_L an o/p voltage V_o is obtained across it.

For -ve half cycle Diode D_1 and D_3 are forward biased and diodes D_2 and D_4 are ~~forward~~ ^{reverse} biased. Therefore D_1 and D_3 will conduct current across them.



DATE / /
PAGE No. 20

But diodes D_2 and D_4 will not conduct. The direction of current shows - Due to current through R_2 an o/p voltage V_o is obtained across it.

PIV of Bridge Rectifier


$$+V_m - V_o = 0$$

$$V_o = V_m$$

Now $-V_o + PIV = 0$

$$PIV = V_o$$


$$\boxed{PIV = V_m}$$

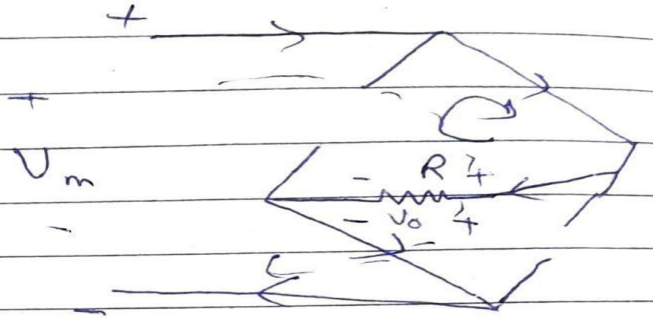


Clipper CKT

→ Clipper is a ckt which cut some specific amount of wave form.

① Positive Series Clipper:

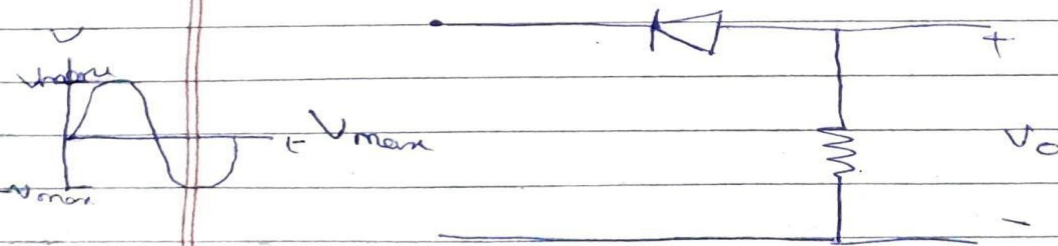



For the half cycle

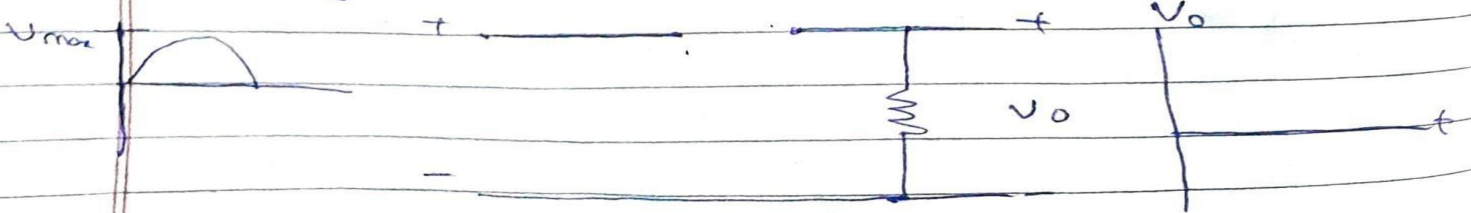



DATE / /
PAGE No. 21

For -ve half cycle

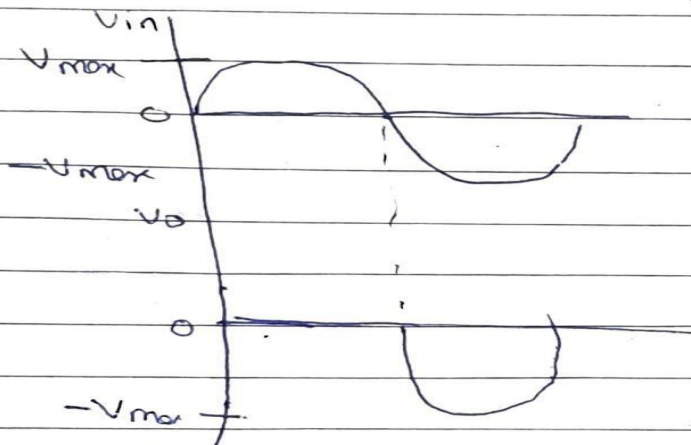
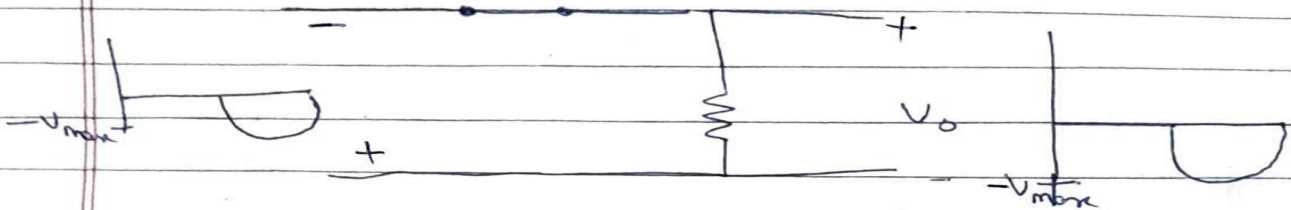


For +ve half cycle n side of diode connect to +ve
So diode become reverse biased (Open ckt). So there
is 0 voltage at o/p.

For -ve half cycle n side of diode connect to -ve
So diode become forward biased (Short ckt) so there
is -Vmax voltage at o/p.

②


Positive Shunt Clipper!

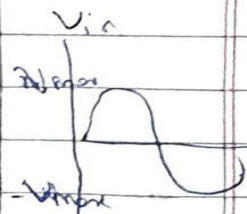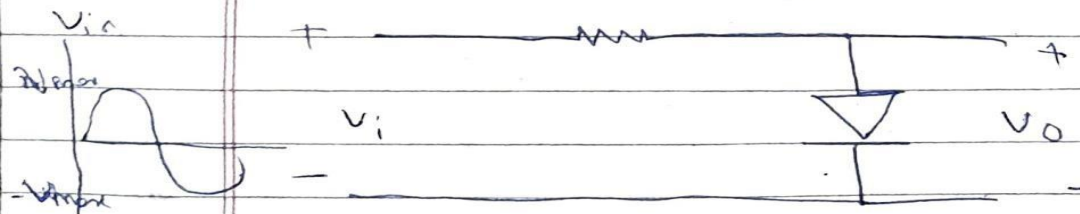





DATE / /
PAGE No. 22

For +ve half cycle

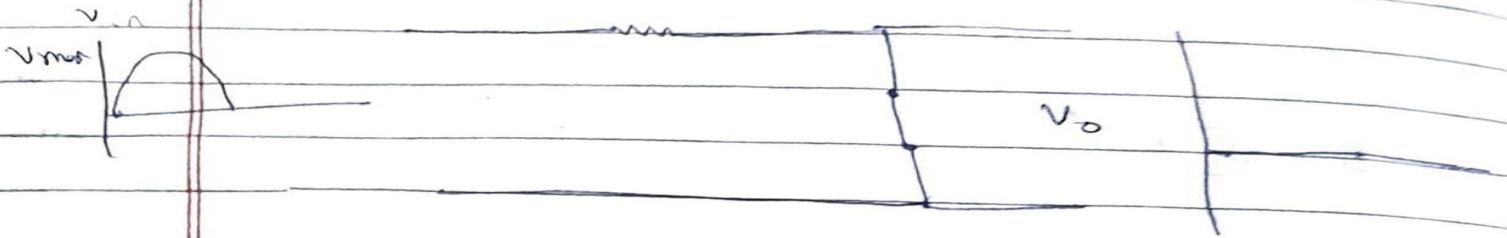

For -ve half cycle

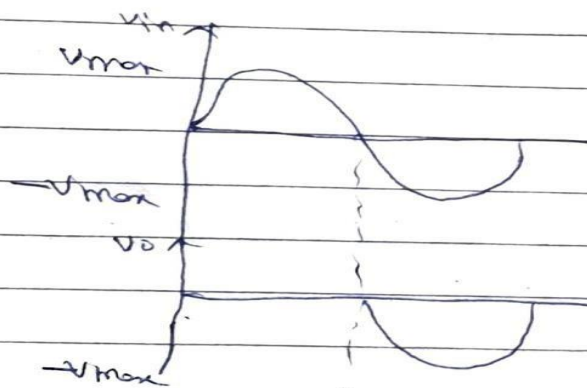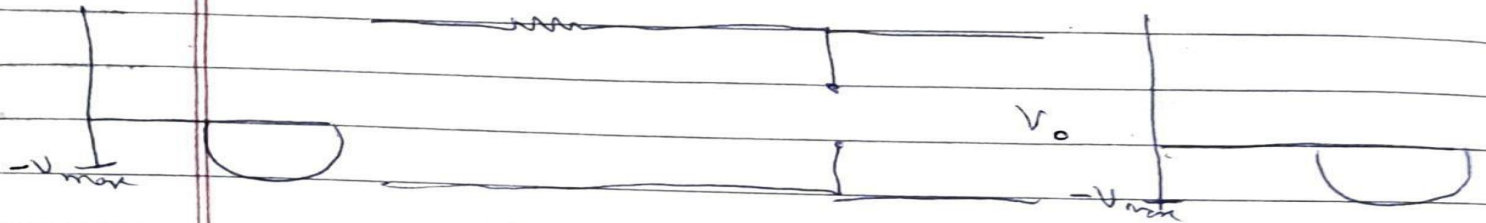

For the half cycle p side of diode connect to the so diode work as a short-ckt. and there is no voltage at o/p


For -ve half cycle p side of diode connect to -ve so diode work as a open ckt and there is $-V_{max}$ at o/p

③ Negative Series Clipper:




DATE / /



PAGE No. 23

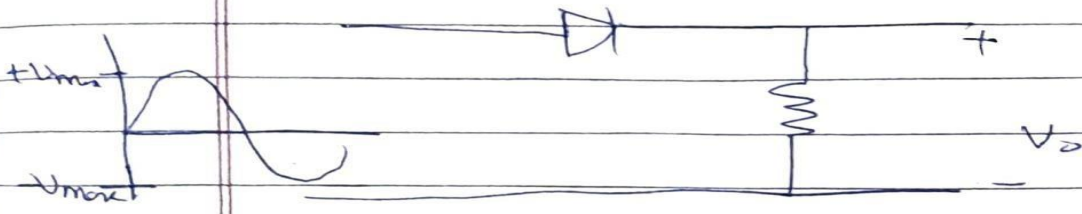

For the half cycle

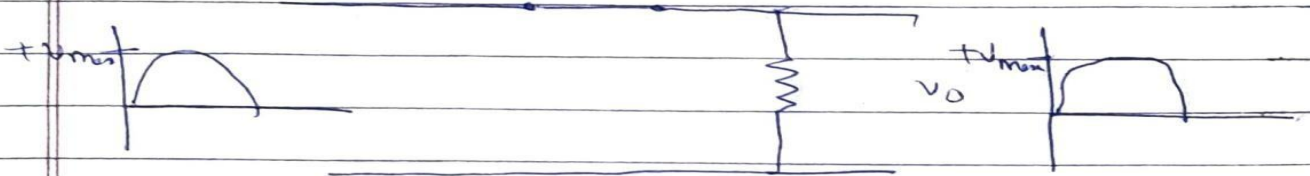


For the half cycle

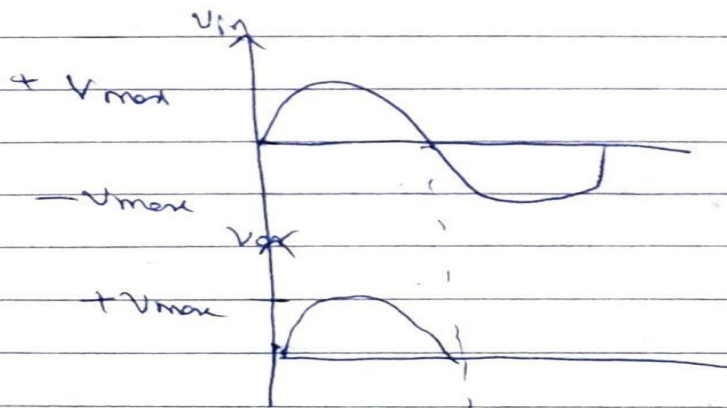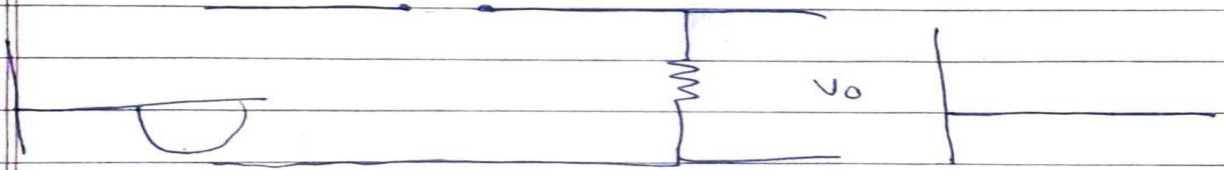

For the half cycle p side of diode connect to the terminal so diode ~~become~~ ^{act as} a short ckt and there is $+V_{max}$ voltage at o/p

For the half cycle n side of diode connect to -ve terminal so diode act as a O.c. and there is 0 voltage at o/p



4) Negative shunt clipper:

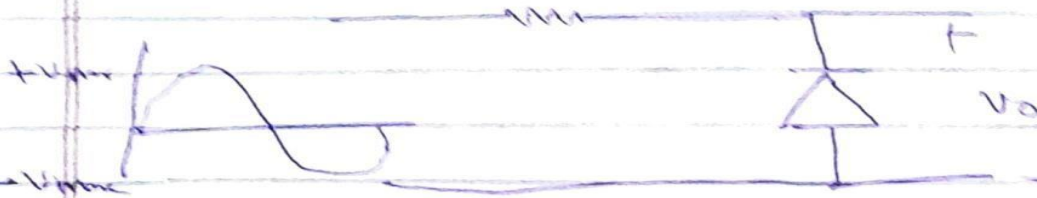

For the half cycle



For the half cycle

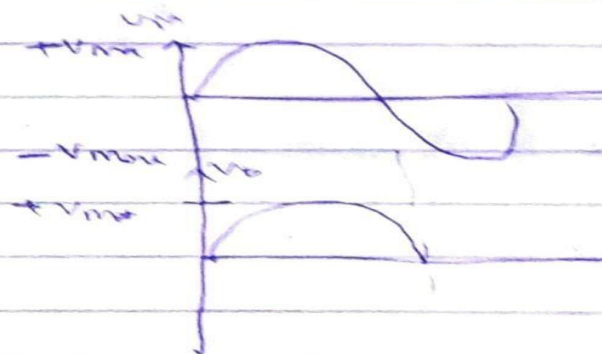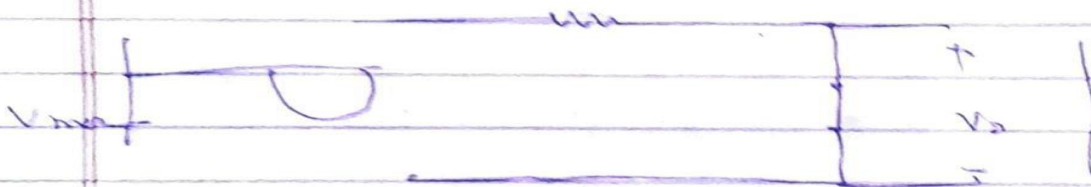


For the half cycle n side of diode connect to the so diode act as a o.c. and $+V_{max}$ voltage get across it.

For $-ve$ half cycle n side of diode connect to $-ve$ so diode act as a s.c. and 0 voltage get across.




Date / /
Page No. 25

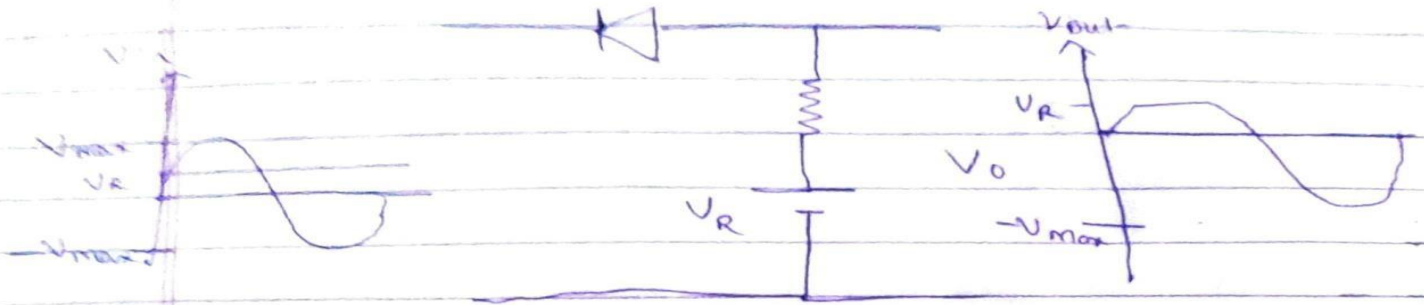5) Positive Voltage Clipper with Positive Bias:




For +ve half cycle

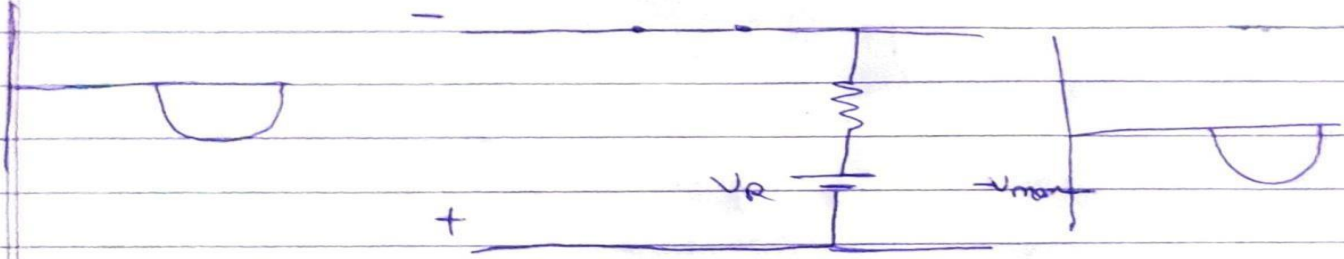


For + half cycle

Case I st $V_R > V_{in}$

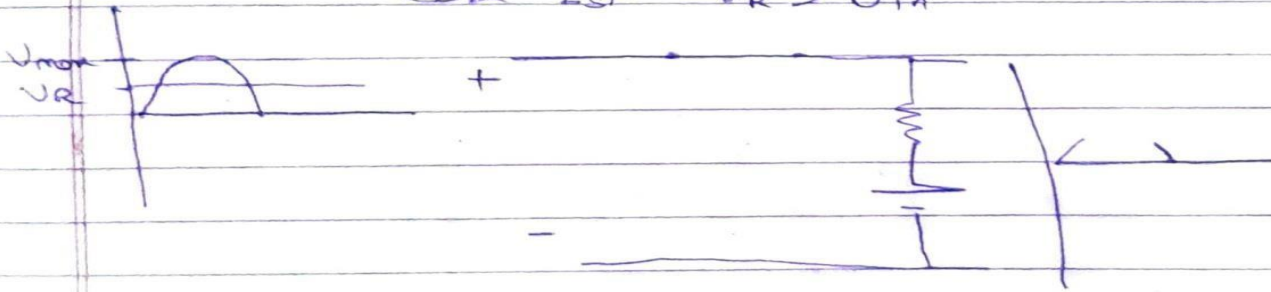

Case II nd $V_R < V_{in}$

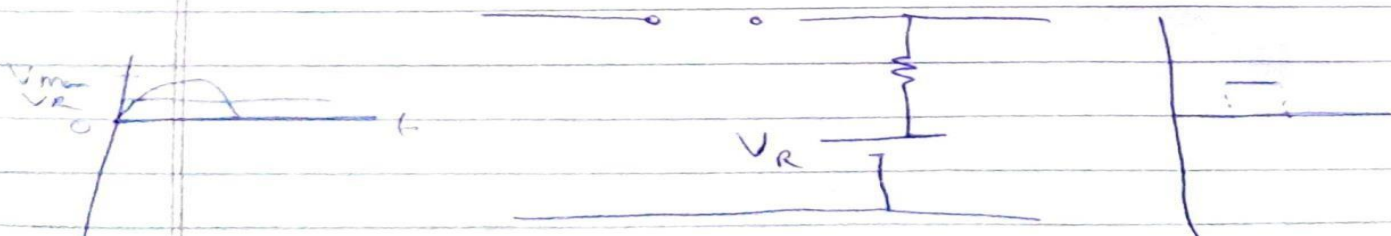

For -ve half cycle n side of diode connect to -ve terminal so diode act as a ~~short~~ ^{open} circuit and there is ~~no~~ ^{input} terminal in put voltage get across it



Date: / /
Page No: 26

For the half cycle when $V_e < V_{in}$ the diode will be a short circuit and input voltage upto V_e get at the o/p
 when $V_e > V_{in}$ the diode work as a.c. and V_e voltage get at the o/p

(c) Positive ~~Series~~ Series clipper with negative biasing



For the half cycle



For -ve half cycle

Case I $V_e < V_{in}$



Case II $V_e > V_{in}$






DATE / /
PAGE No. 27


When $V_R < V_{in}$ then n side of diode at higher potential and p side of diode at lower potential than diode work as a o.c. and $-V_R$ voltage get at the o/p. For $V_R > V_{in}$ n side of diode at lower potential and p side of diode at higher potential than diode work as a S.c. and $-V_{max}$ voltage get at the o/p

⑦

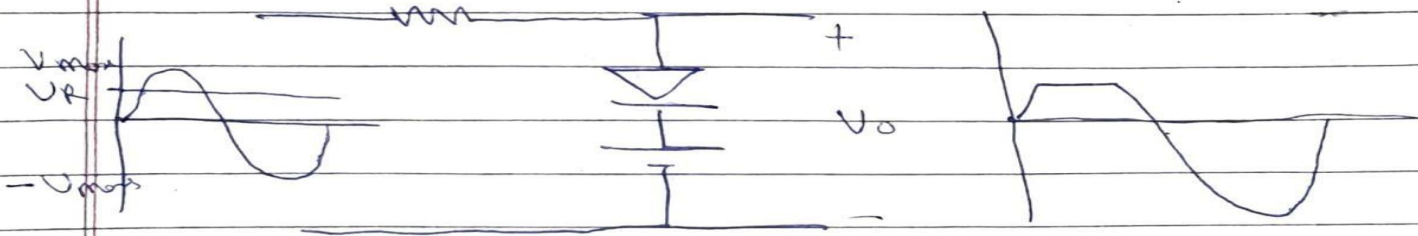
Positive Shunt clipper with positive biasing



$V_{in} < V_R$

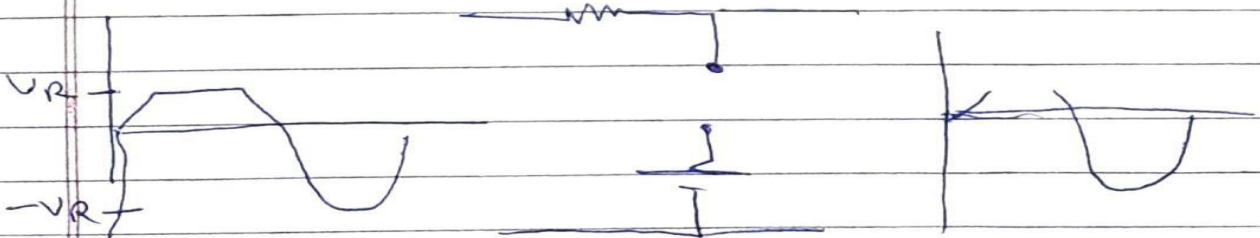

$V_{in} > V_R$

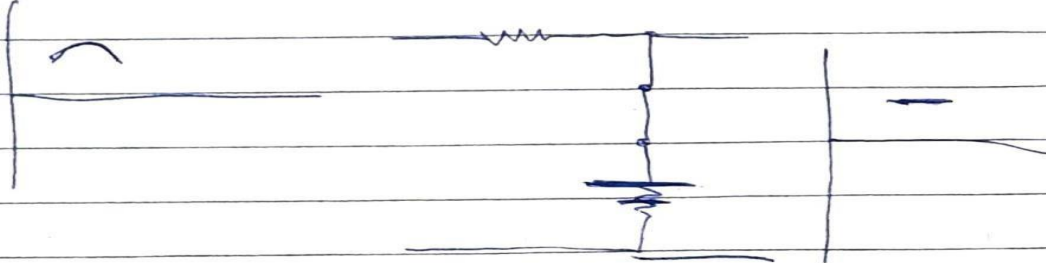


When $V_{in} < V_R$ then n side of diode at higher potential and p side of diode at lower potential




DATE / /
PAGE No. 28

These diodes work as a o.c. and total V_p voltage get at the o/p.
For $V_{in} > V_p$ n side of diode at lower potential and p side of diode at higher potential then diode act as a s.c. and V_p voltage get at the o/p.

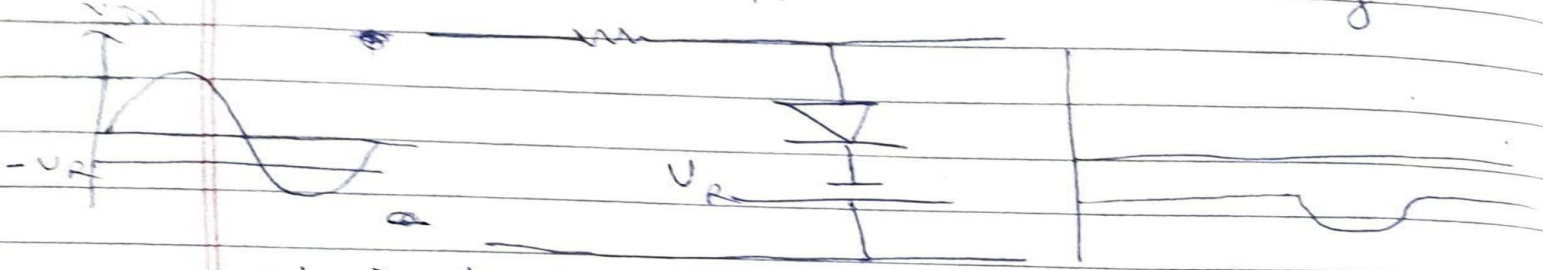
⑧ Positive Shunt clipper with +ve Biasing



$V_{in} > V_p$

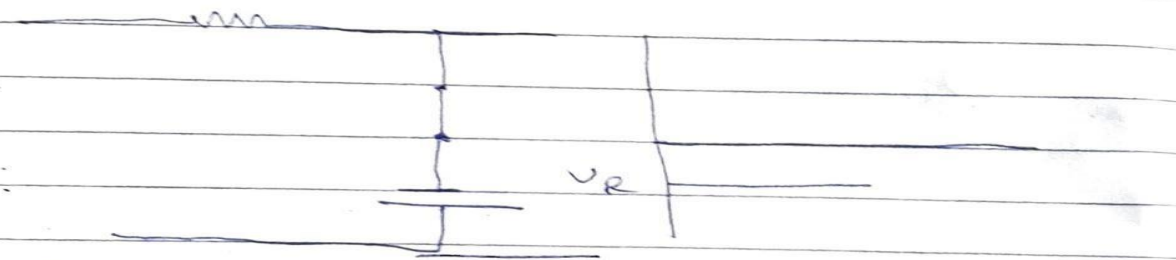

$V_{in} < V_p$

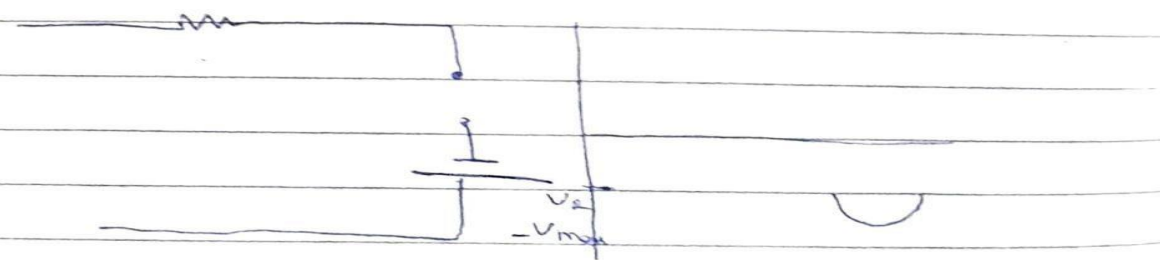

For $V_{in} > V_p$ diode work as a s.c. then p side of diode connect to ^{higher potential} ~~terminal~~ then diode act as a s.c. so V_p voltage get at the o/p

For $V_{in} < V_p$ n side of diode connect to higher potential then diode act as a o.p so total




DATE / /

PAGE NO. 29


V_{in} voltage get at the o/p.

Q


Negative Series clipper with +ve Biasing

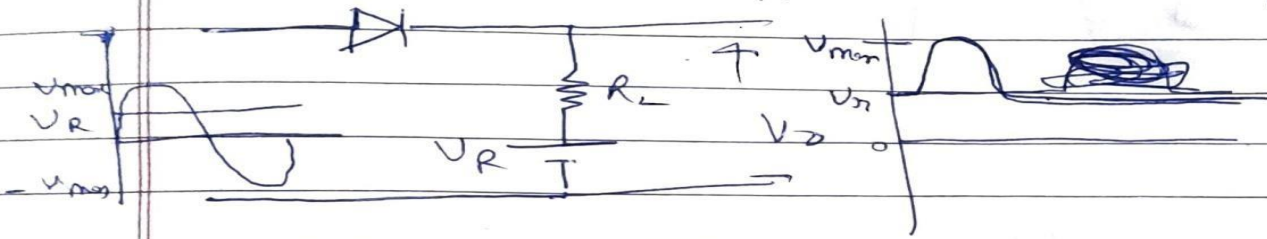

$V_{in} > V_R$

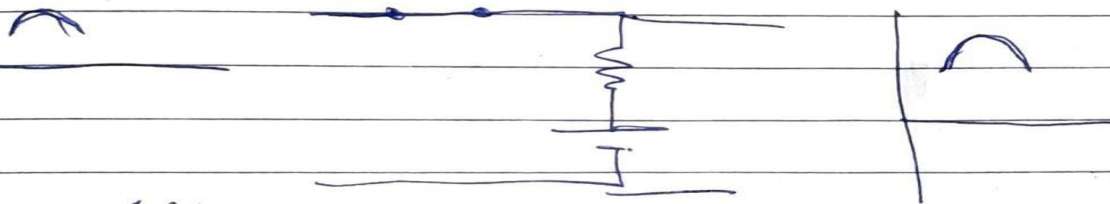

$V_{in} < V_R$

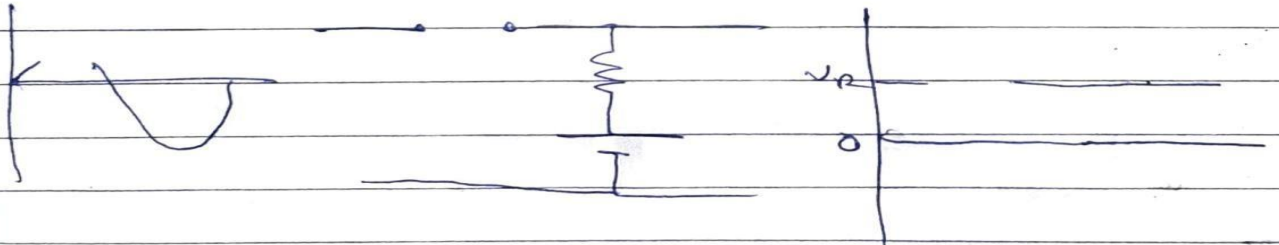





For $V_{in} > V_R$ +ve side of diode at higher potential than diode act as a s.c. then total V_{in} voltage get at the o/p

For $V_{in} < V_R$ +ve side of diode at lower potential than diode act as a o.c. so V_R voltage get at the o/p.



DATE / /
PAGE NO 30

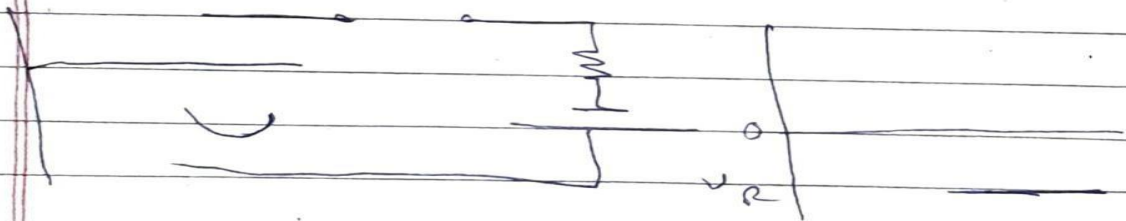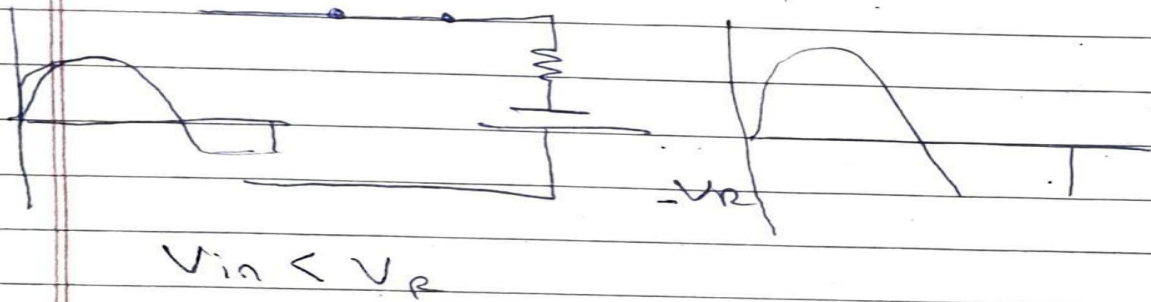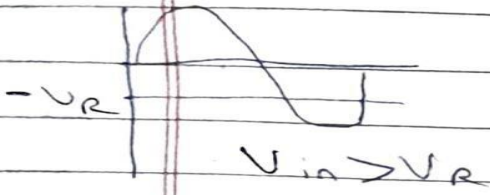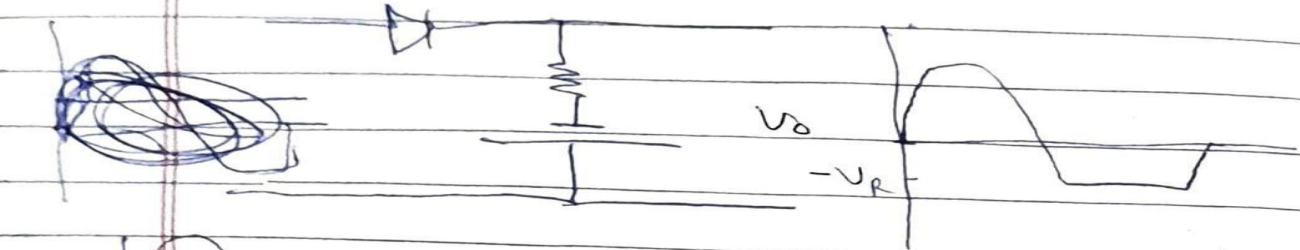(10) Negative Sense Clipper with $-V_R$ Bias:



For $V_{in} > V_R$ p side of diode at higher potential so diode act as a s.c. and total i/p voltage get at the o/p.

For $V_{in} < V_R$ p side of diode at lower potential so diode act as a o.c. and total V_R voltage get at the o/p.



DATE / /


PAGE No. 31

(11)


Clippers
+ve Shunt, with the Bias



$$V_{in} > V_R$$

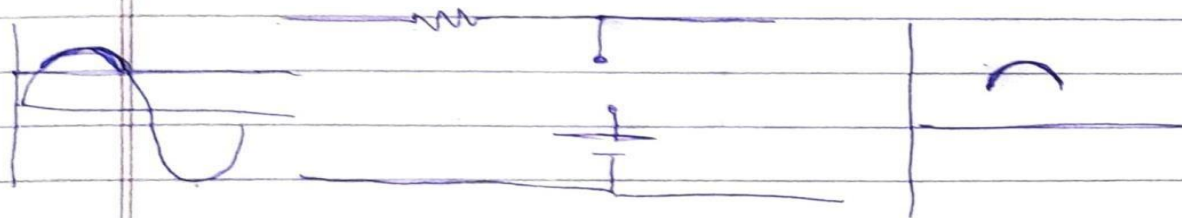

$$V_{in} < V_R$$

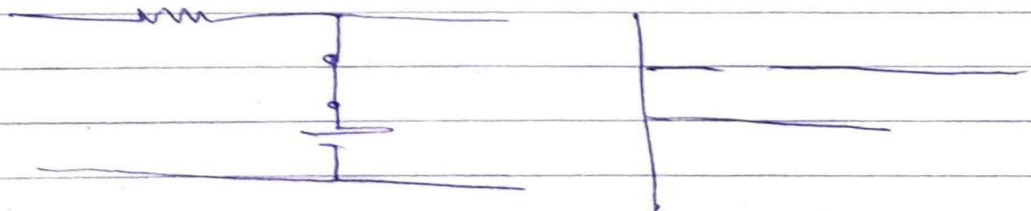


For ~~the~~ ~~both~~ ~~cases~~ $V_{in} > V_R$ the p side of diode at lower potential than diode act as o.c and total i/p voltage gets at the O/P.

For $V_{in} < V_R$ the p side of diode at higher potential than diode act as a s.c. and V_R voltage gets at the O/P




DATE / /
PAGE NO. 32

12) -ve Shunt clipper with -ve bias

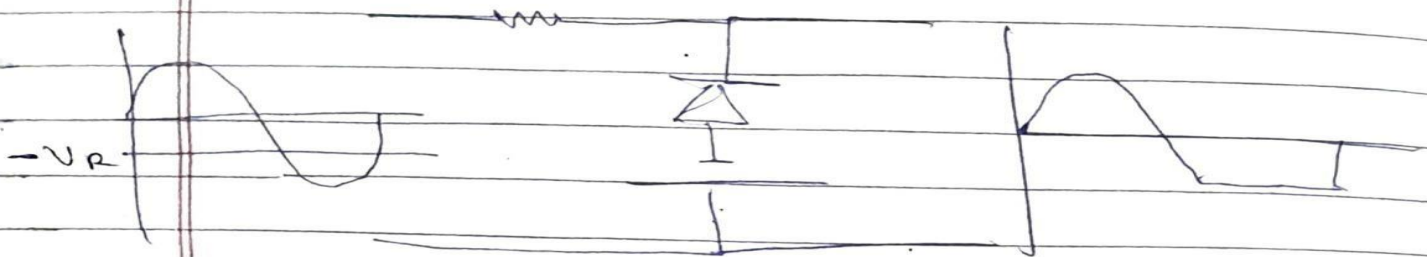

For $V_{in} > V_R$

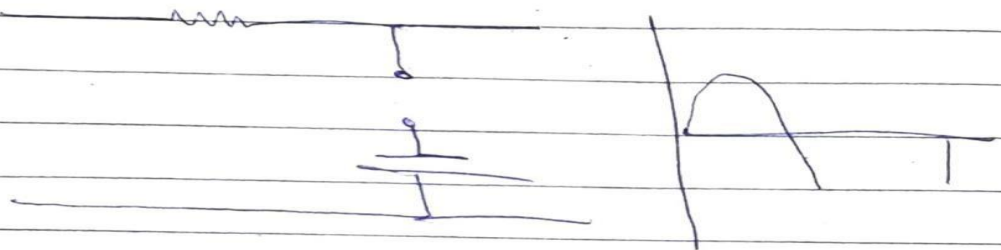

For $V_{in} < V_R$



For $V_{in} > V_R$ p side of diode at lower potential than diode act as a o.c. and total i/p voltage get as the o/p.


For $V_{in} < V_R$ p side of diode at higher potential than diode act as a s.c. and V_R voltage get at the o/p.




DATE / /
PAGE No. 33

13

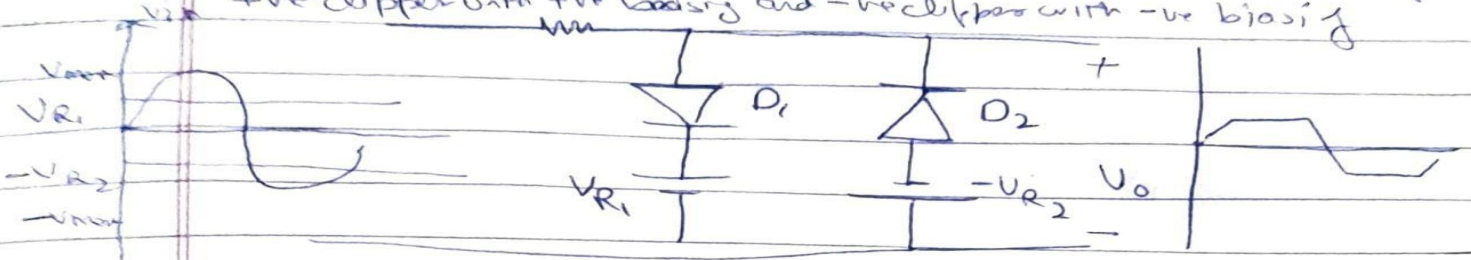
Combination clipper ckt: - It is a combination of the clipper with the biasing and -ve clipper with -ve biasing




For the half cycle and $V_{R1} > V_{in}$

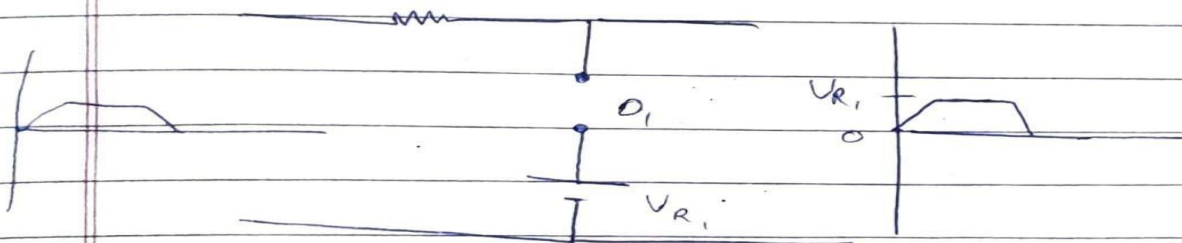


For the half cycle and $V_{R1} < V_{in}$

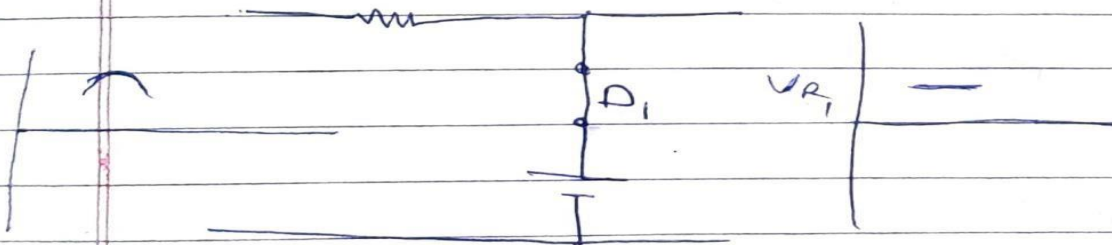

For -ve half cycle and $V_{R2} > V_{in}$

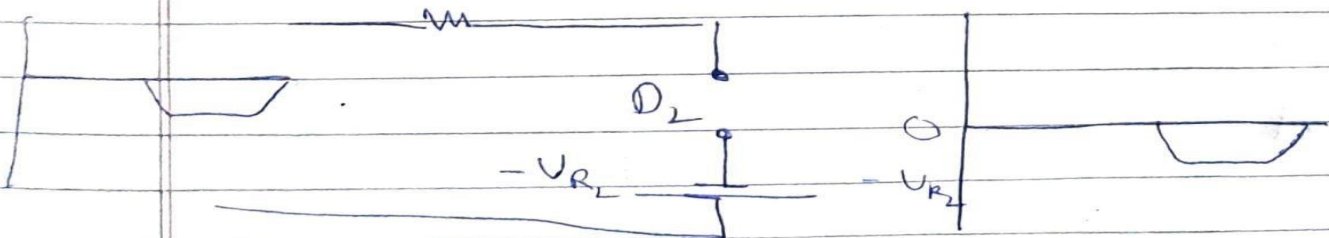

For -ve half cycle and $V_{R2} < V_{in}$

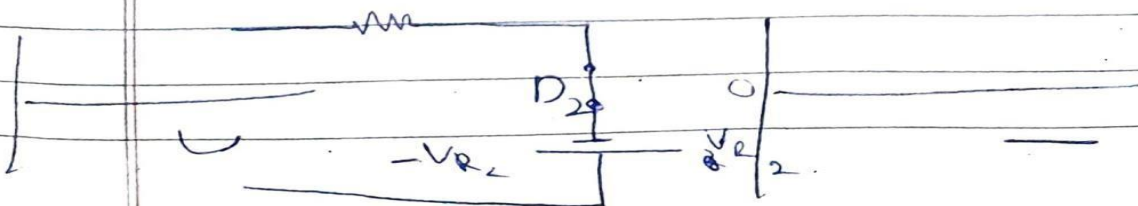





DATE / /
Page No. 34

h.w


Q Draw o/p wave form of the given ckt :-

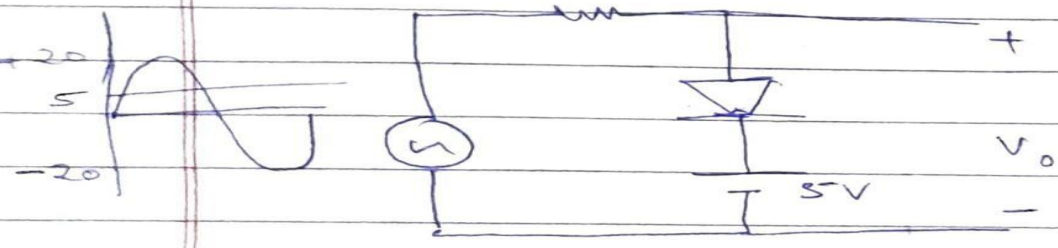


Sol For $V_{in} < V_R$

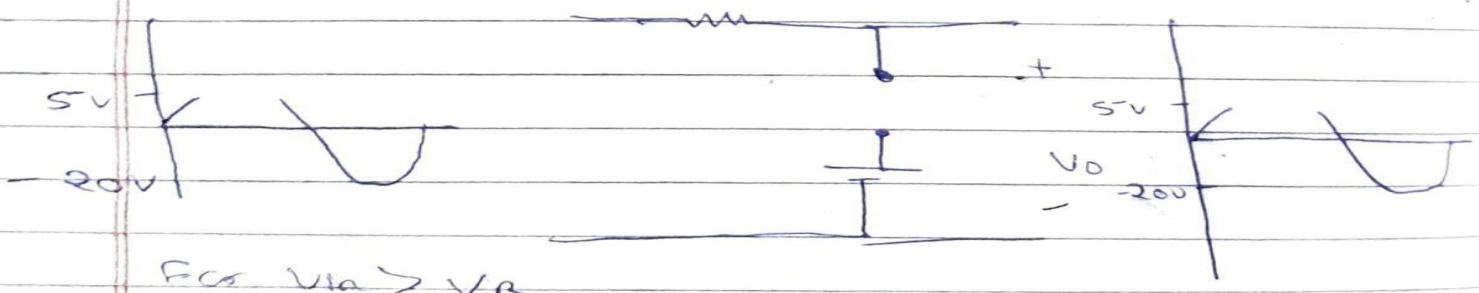

For $V_{in} > V_R$

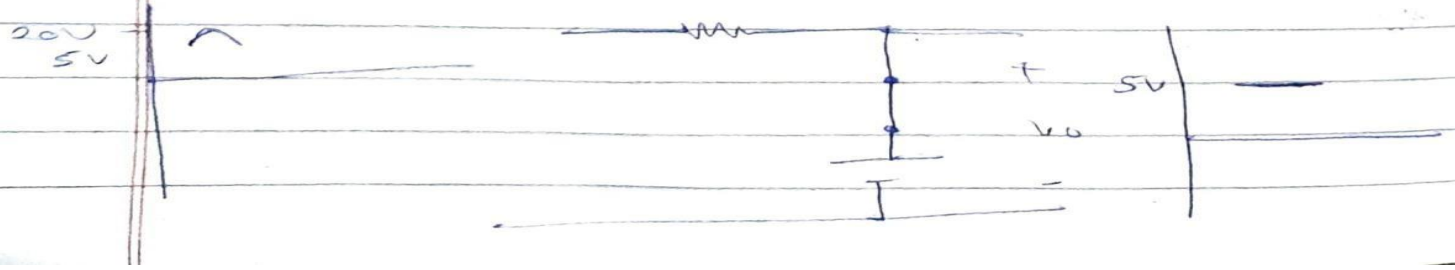

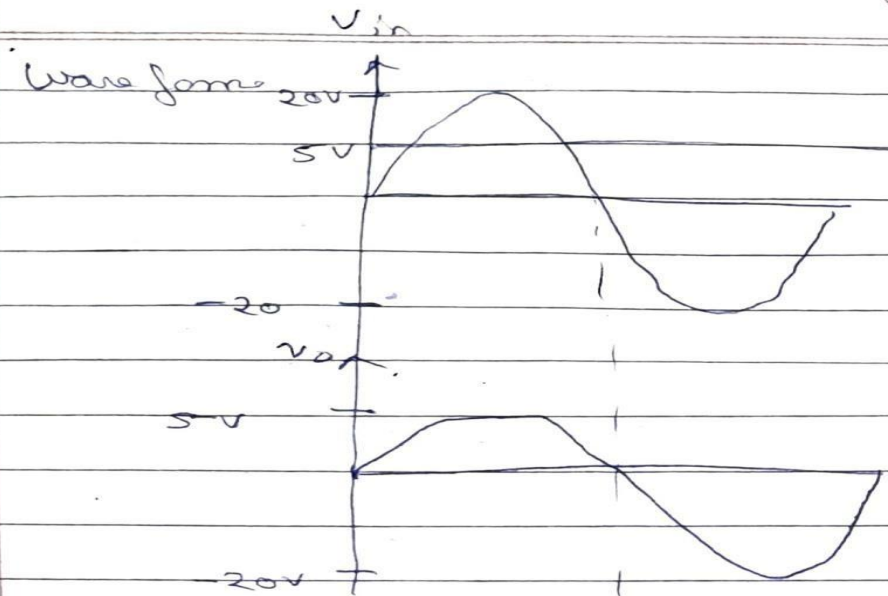


Zener diode



It is a highly doped p-n junction diode which is always works in reverse biased after breakdown.

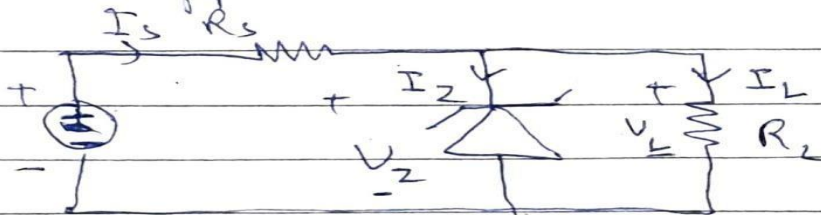The most important application of zener diode is Zener diode as a voltage regulator. The circuit of this application are shown in the fig




According to the fig load voltage V_L is always equal to V_Z



DATE / /
PAGE No. 36

Q Find V_L , V_S , I_Z , I_S

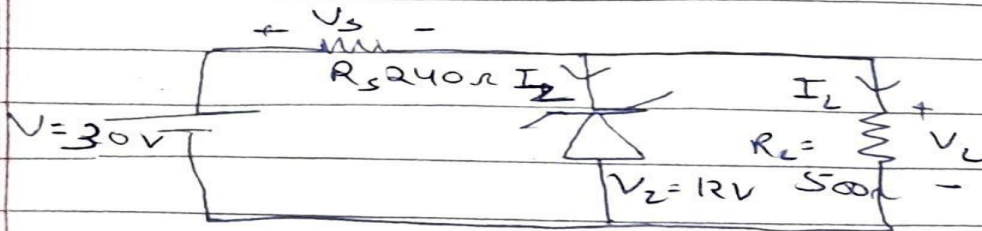

Sol

$$V_Z = V_L = 12V$$

~~$$-30 + I_S R_S +$$~~

$$-30 + V_S + 12 = 0$$

$$V_S = 30 - 12 = 18V$$

$$I_S = \frac{V_S}{R_S} = \frac{18}{240} = 0.075A$$

Now


$$I_S = I_Z + I_L$$

$$0.075 = I_Z + \frac{12}{500}$$

$$0.075 = I_Z + 0.024$$

$$I_Z = 0.075 - 0.024 = 0.051A$$

Q Find I_Z

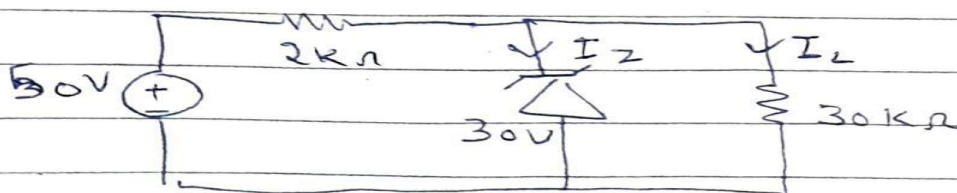



Date / /
Page No. 37

Sol

$$V_L = 30V$$

$$I_L = \frac{30}{30000} = 0.001 A$$

$$V_S = 20V$$

$$I_S = \frac{20}{20000} = 0.001 A$$

$$I_S = I_2 + I_L$$

~~$$I_2 = 0$$~~

$$I_2 = I_S - I_L$$

$$= 0.010 - 0.001$$

$$= 0.009 A$$

$$I_2 = 9 mA$$

Voltage multiplier

Voltage multiplier is a ckt which give n multiple of i/p voltage at o/p i.e.

if V_{in} is i/p then $V_o = nV_{in}$


where n is the natural number so

$$V_o = 2V_{in}, 3V_{in}, 4V_{in} \dots$$

Voltage Doubler ckt




For the half cycle

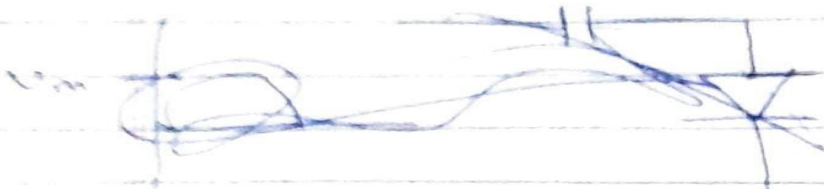

For the half cycle diode D_1 act as a S.e.c and D_2 act as a o.p. So path of current shown in the fig and our capacitor C_1 get charge upto V_m

$$V_{C1} = V_m$$

For -ve half cycle

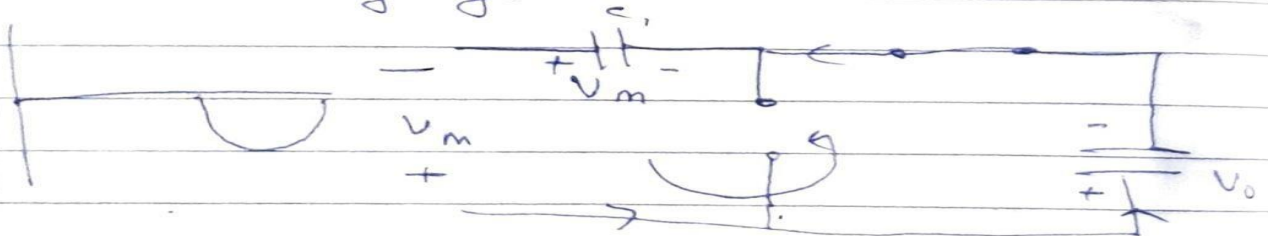

For -ve half cycle diode D_1 act as a o.p.c and D_2 act as a S.e. So path of current shown in the fig and now C_1 capacitor become discharge and C_2 capacitor become charge so the voltage in C_2 is


$$-V_m - V_m + V_o = 0$$

$$\text{So } V_o = 2V_m$$




DATE / /
PAGE No. 39

Voltage Tripler CKT

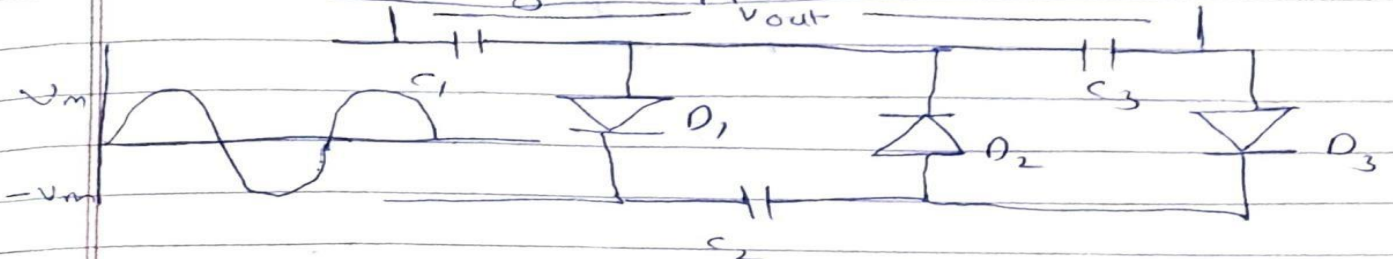

For +ve half cycle

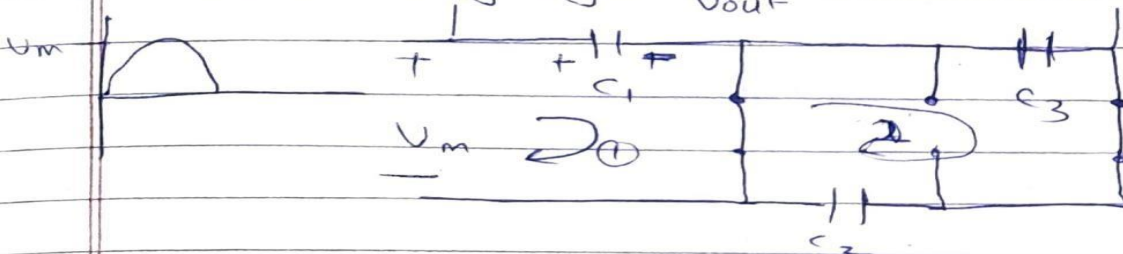


For +ve half cycle diode D_1 and D_3 are S.C. and D_2 is O.P.
Now loop $+V_{C1} - V_m = 0$

$$V_{C1} = V_m$$

So capacitor C_1 charged upto V_m

Now loop C_2 and C_3 are discharged so no voltage at this loop

For -ve half cycle

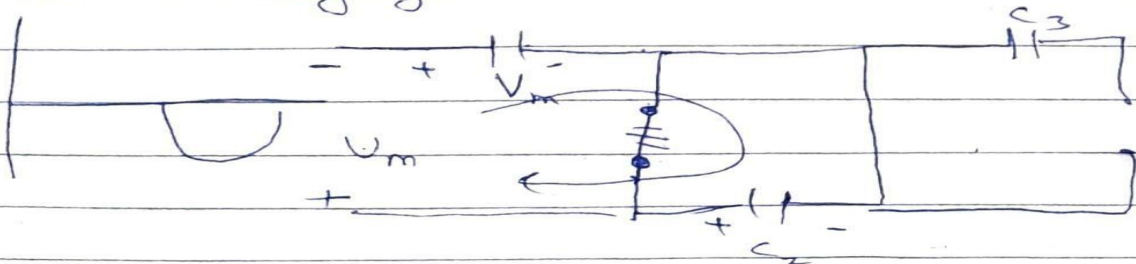

Diode D_1 and D_3 are O.C. and D_2 is S.C.

Now loop $+V_m - V_{C2} + V_m = 0$


$$V_{C2} = 2V_m$$

So capacitor C_2 becomes charged upto $2V_m$ and C_1 becomes discharged upto 0V



Date / /
Page No. 10

Now for 2nd half cycle v_o

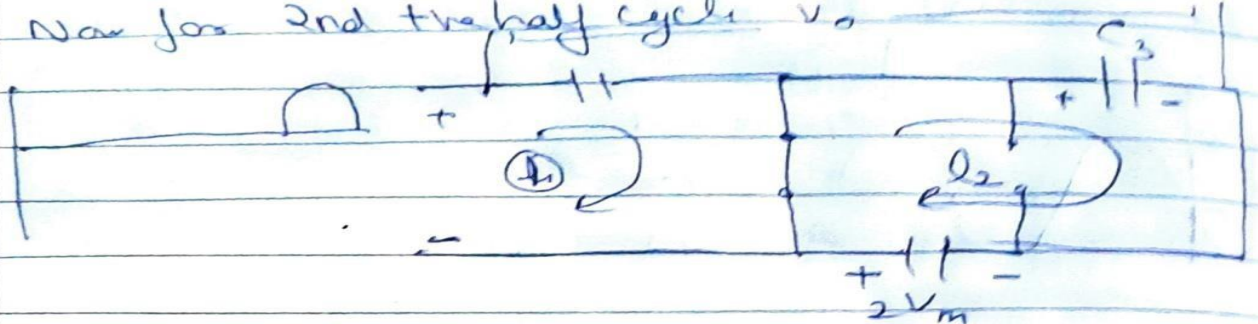

D_2 and D_3 s.c. and D_2 o.r. So

Loop 1

$$V_{c1} = V_m$$

Loop 2 = $V_{c2} - V_{c3} = 0$


$$V_{c3} = 2V_m$$

So total o/p voltage is


$$V_{c1} + V_{c3} = 3V_m$$

Clamper :-

① Position clamper :-

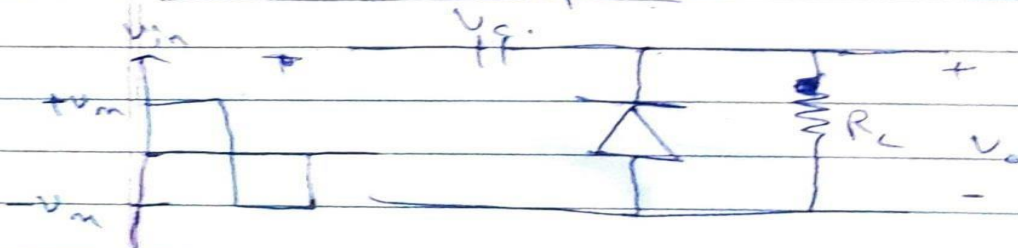

For ~~+~~ half cycle

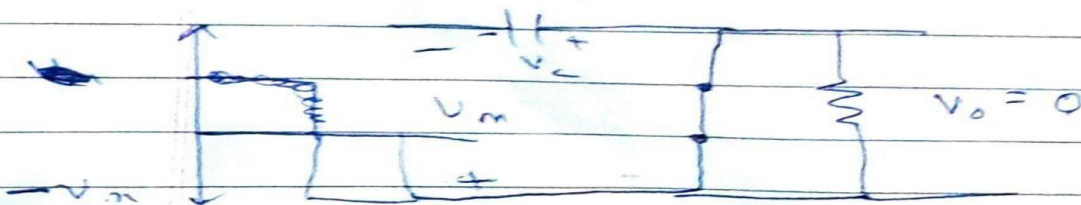




Date / /
Page No. 41

D → S.C.

$$-V_m + V_c = 0$$

$$V_c = V_m$$


For the half cycle

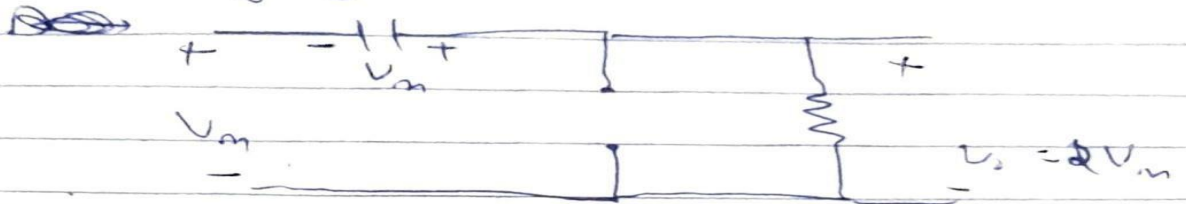


D → O.C.

$$V_m + V_m + V_c = 0$$

$$V_o = 2V_m$$

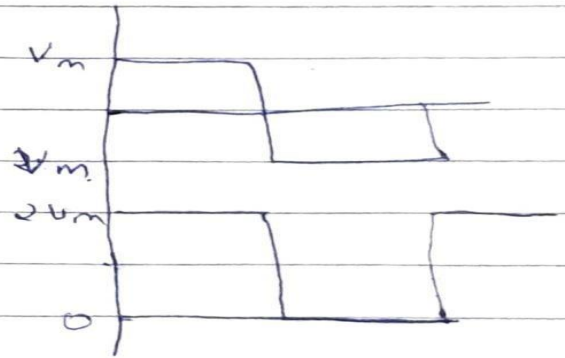


② -ve clamper:

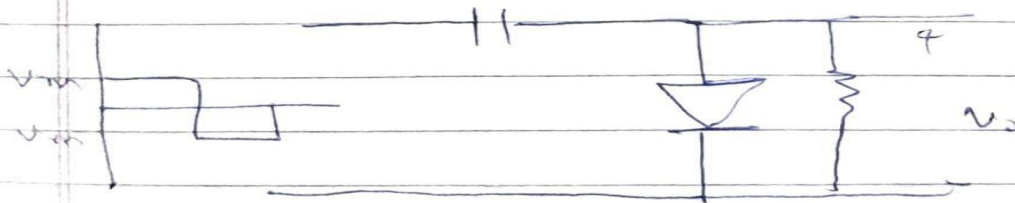

For the half cycle

D → S.C.

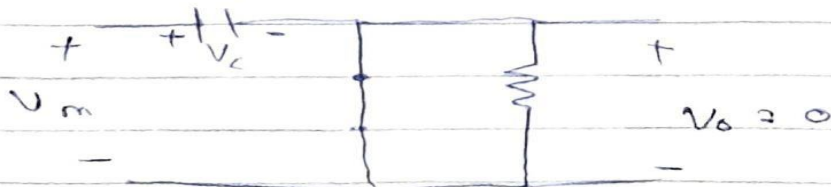

$$-V_m + V_c = 0$$


$$V_c = V_m$$



DATE / /
PAGE No. 42


For $-ve$ half cycle

$D \rightarrow O.P.$

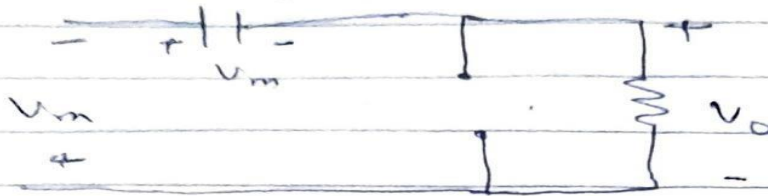


$$+V_m + V_m + V_o$$

$$V_o = -2V_m$$

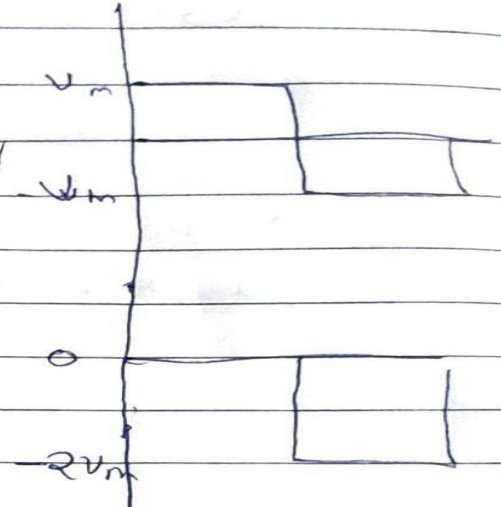


③

Positive clamper with $+ve$ biasing:-

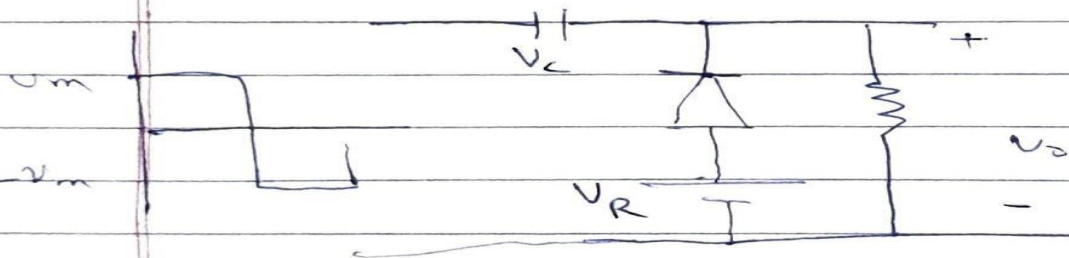

For $-ve$ half cycle:-

$D \rightarrow S.C.$

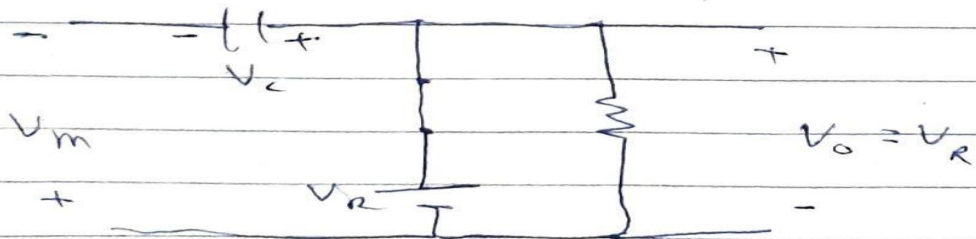

$$-V_m - V_r + V_c = 0$$

$$V_c = V_m + V_r$$




DATE / /

PAGE No. 43


For the half cycle

$D \rightarrow O.C.$

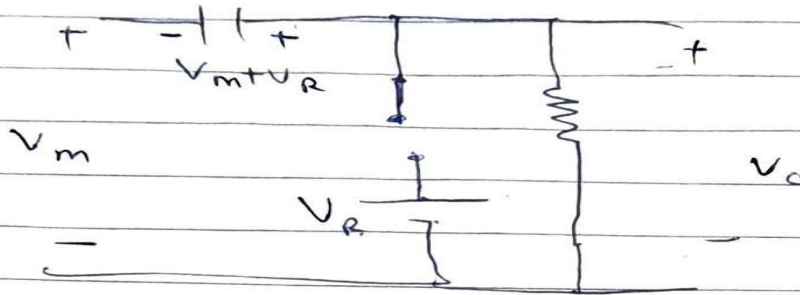


$$+V_m + V_m + V_R \rightarrow V_o = 0$$


$$V_o = 2V_m + V_R$$

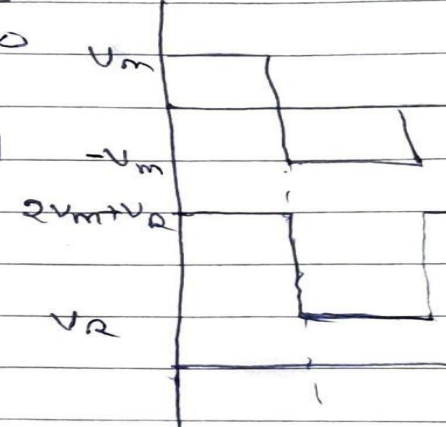

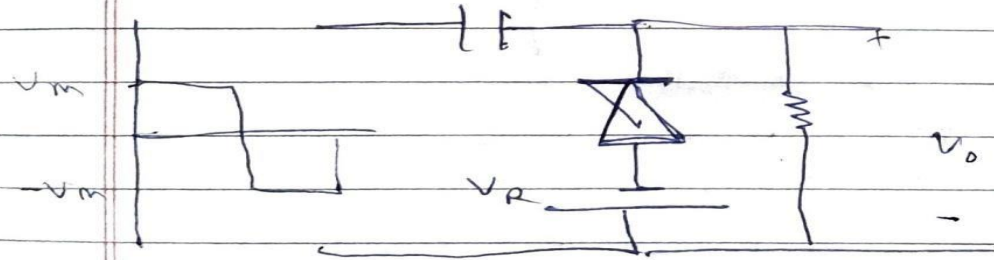9) Positive clamper with $-V_c$ biasing:-



For the half cycle $D \rightarrow S.C.$

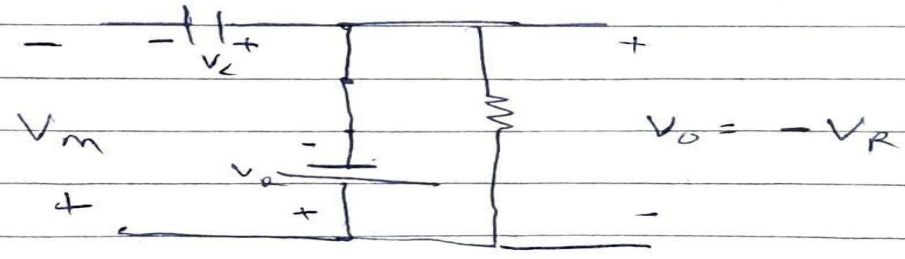


$$V_m - V_c - V_R = 0$$

$$V_c = V_m - V_R$$




DATE / /
PAGE No. 44

For the half cycle $D \rightarrow O.C.$

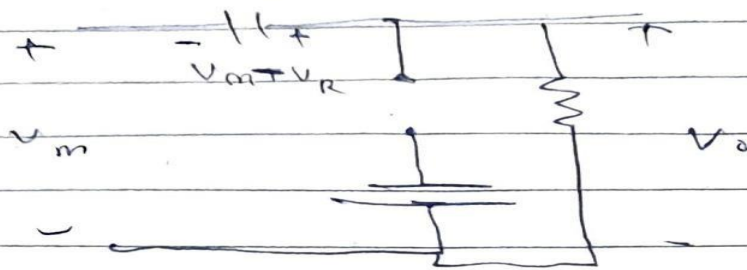


$$V_m + V_m - V_R + V_o = 0$$


$$V_o = 2V_m - V_R$$

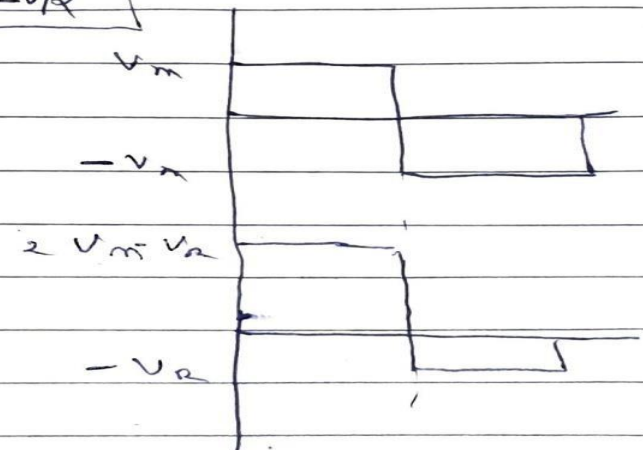

(S) -ve clamper with the biasing

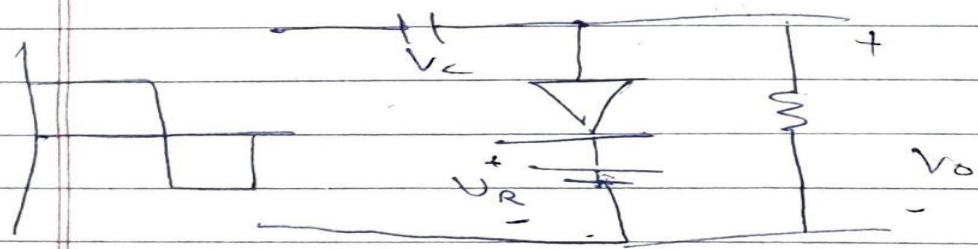

For the half cycle $D \rightarrow S.C.$

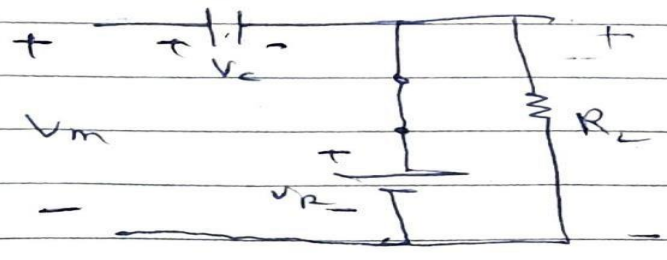

$$V_m - V_c + V_R = 0$$


$$V_c = V_m + V_R$$

$$V_o = V_R$$




DATE / /
PAGE NO. 45

For -ve half cycle D.O.P

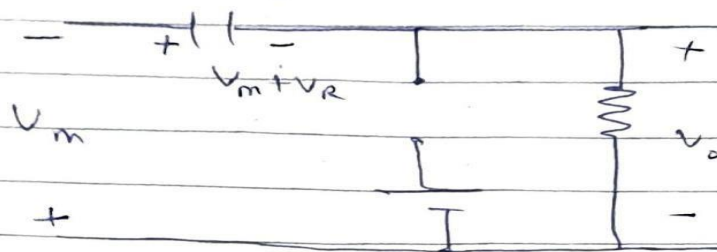


$$V_m + V_m + V_R + V_o = 0$$

$$V_o = -(2V_m + V_R)$$

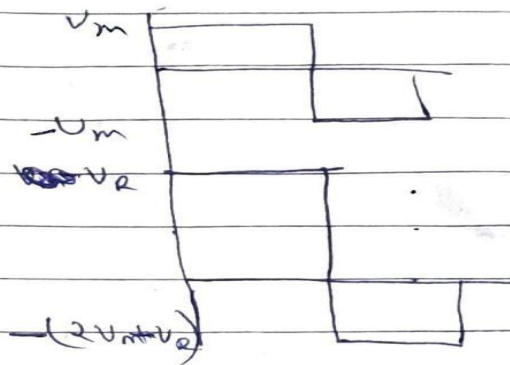

⑤ -ve clamper with +ve biasing:

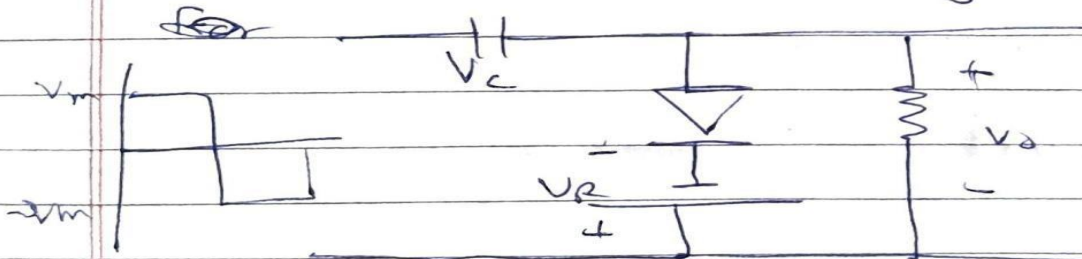

For the half cycle D.S.C.




$$V_m - V_c + V_R = 0$$

$$V_c = V_m + V_R$$



Date / /
Page No. 46

For -ve half cycle O.O.P

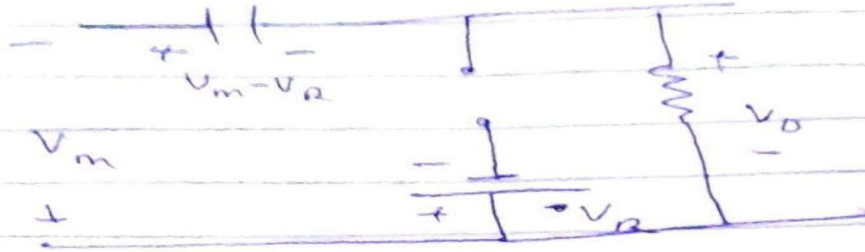

$$V_m + V_m - V_R + V_o = 0$$

$$V_o = -(2V_m - V_R)$$

