



### Unit 3

#### Syllabus

Operational Amplifiers: Introduction, Op-Amp basic, Practical Op-Amp Circuits (Inverting Amplifier, Non-inverting Amplifier, Unit Follower, Summing Amplifier, Integrator, Differentiator). Differential and Common-Mode Operation, Comparators.



PAGE No. 1  
DATE: / / 202

### Unit 3


### Operational Amplifier (Op-Amp)

An op-amp is a high gain ( $10^5 - 10^6$ ) amplifier which is used to perform variety of operations such as amplification, addition, subtraction, differentiation, integration etc.

### Advantages of ~~op~~ op-amp


- It has smaller size
- It has less power consumption
- It is easy to replace
- Low cost
- High reliability

### Symbol and terminals

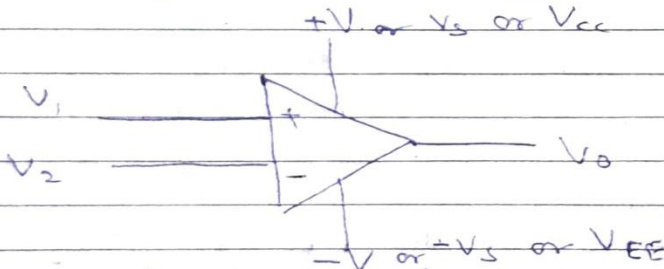

- The non-inverting i/p terminal marked as +
- The inverting i/p terminal marked as -
- The positive supply voltage +V
- The negative supply voltage -V
- The o/p terminal Vo

### Non inverting i/p terminal

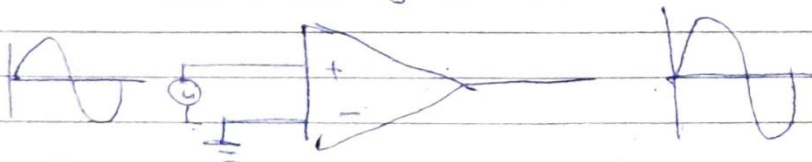


If we connect the i/p s/g to the non-inverting terminal, then the amplified o/p s/g is in phase with the i/p s/g.




PAGE: 2  
DATE: / /

Inverting i/p terminal

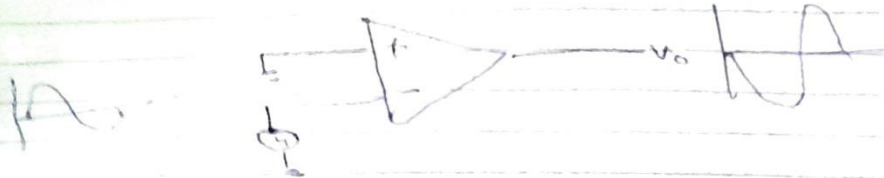

If we connect the i/p s/g to the inverting terminal then the amplified o/p s/g is  $180^\circ$  out of phase w.r.t. the i/p s/g.

Block diagram of opamp

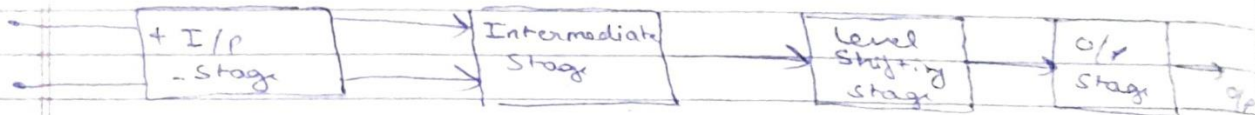

It basically consists of 4 stages:

①

I/p stage: It consists of a dual i/p and dual o/p differential amplifier.

The 2 i/p are non-inverting and inverting i/p terminals. The stage provides most of the voltage gain of opamp. This stage decides the value of i/p resistance ( $R_i$ ).

②

Intermediate stage: It consists of a dual i/p and ~~single~~ <sup>single</sup> o/p differential amplifier.

It is driven by the o/p of i/p stage. I/p stage alone can't provide high gain so intermediate stage provides the required additional voltage gain.

③

Level shifting stage: As opamp amplifier the dc s/g slips and in different cascading stages coupling capacitors are not used hence stage by stage dc level  $\uparrow$  w.r.t. above the ground potential.

Level shifting stage is used the intermediate stage to shift the dc level to 0 V w.r.t. ground.



- ④ O/p stage : This stage ↑ the o/p voltage and raises the current carrying capability of op amp. It also provides low o/p impedance.


### Modes of opamp

An op amp can work in 3 modes :-


- ① Single ended mode
- ② Double ended mode or ~~different~~ differential mode
- ③ Common mode

- ① Single ended mode :- If the i/p s/g is applied only one of the i/p terminals and other i/p terminal is connected to ground, then op-amp is said to be operation in the single ended mode.

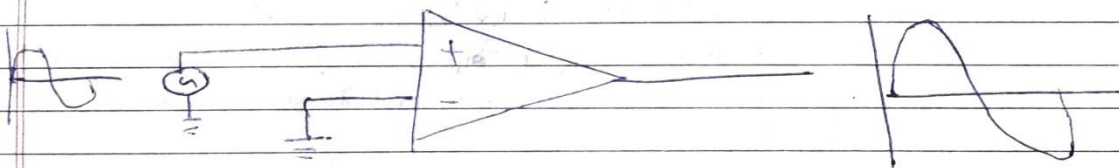- (a) If we connect the i/p s/g to the NI terminal then the amplified o/p s/g is in phase with the i/p s/g.



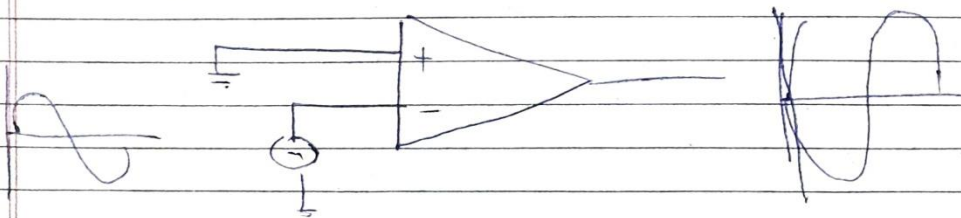- (b) If we connect the i/p s/g to the I terminal then the amplified o/p s/g is 180° ~~phase~~ out of phase with the i/p s/g.



- ② Differential mode : In this mode of operation i/p s/g is applied at both the i/p terminals of opamp. The o/p voltage is directly proportional to the difference b/w 2 i/p voltages is


$$V_o \propto V_1 - V_2$$

$$V_o = A_d(V_1 - V_2)$$






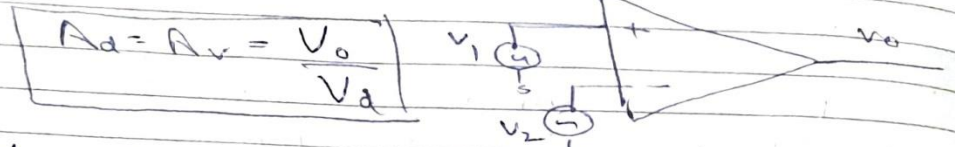Where  $A_d$  is constant of proportionality and is called differential voltage gain or open loop gain ( $A_v$ ) and  $V_1 - V_2 = V_d$  is called differential voltage  
so



③

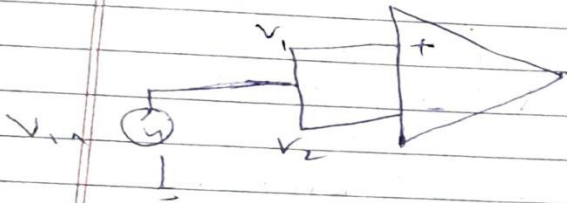**Common mode :-** In this mode same i/p s/g is applied to both the i/p terminals i.e.  $V_1 = V_2 = V_{in}$



So ideally for  $V_o = A_d(V_1 - V_2) = 0$

But practically o/p voltage  $V_o$  is proportional to common mode s/g  $V_c$  where  $V_c = \frac{V_1 + V_2}{2}$

i.e.  $V_o \propto V_c$

$$V_o = A_c V_c$$

where  $A_c$  is constant of proportionality and is called common mode gain. Thus we find that even if  $V_1 = V_2$ , there exist some finite o/p voltage practically

The total o/p of any op-amp is

$$V_o = A_d V_d + A_c V_c$$

### Common mode rejection ratio (CMRR)

It is the ability of opamp to reject in common mode s/g and is defined as the ratio of  $A_d$  to  $A_c$  and is denoted by  $\beta$

$$\beta = \frac{A_d}{A_c}$$

Ideally  $A_c = 0$  so  $\beta = \infty$

CMRR is decible

$$CMRR(dB) = 20 \log_{10} \left| \frac{A_d}{A_c} \right|$$



Q For a given opamp  $CMRR = 10^5$  and  $A_d = 10^5$  what is the  $A_c$  for the amplifier?

Sol  $A_c = \frac{A_d}{CMRR} = \frac{10^5}{10^5} = 1$

Q Given that  $CMRR$  is 100000 I/p common mode voltage is 12V differential voltage gain is 4000. Calculate o/p common mode voltage

Sol  ~~$V_o = A_c V_c$~~   $V_c = 12V$


~~$A_d = 4000$~~   $A_d = 4000$

$CMRR = 100000 = \frac{A_d}{A_c} \Rightarrow A_c = 0.04$

$V_o = A_c V_c \Rightarrow 0.04 \times 12$

$V_o = 0.48V$

Characteristics of an ideal opamp

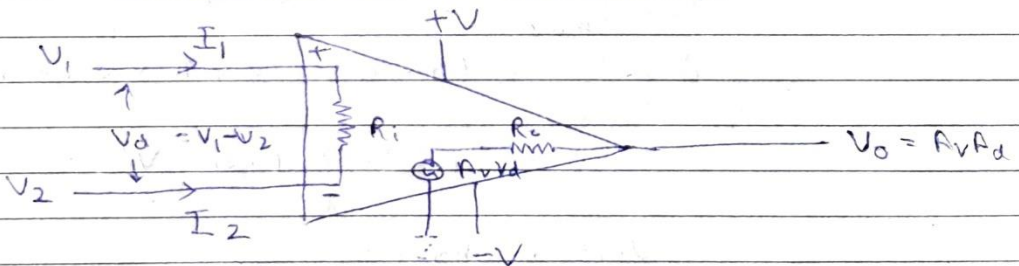

- ①  $\infty$  voltage gain ( $A_v = \infty$ )
- ②  $\infty$  i/p resistance ( $R_i = \infty$ )
- ③ 0 o/p " ( $R_o = 0$ )
- ④ 0 offset voltage (In practical opamp if  $V_1$  and  $V_2$  is 0 then some finite voltage present at o/p. That finite voltage is called offset voltage)
- ⑤  $\infty$  Bandwidth (Bandwidth is the range of freq in which over opamp work as a amplifier)
- ⑥  $\infty$  CMRR





② or slow rate

$$s = \left. \frac{dV_o}{dt} \right|_{\max} = \infty \quad (\text{V/}\mu\text{s})$$

③ A power supply rejection ratio (PSRR = 0)

(PSRR is the change in  $V_o$  when any fluctuation in  $V_{PS}$  is)

④ The output of particular opamp is 8V in 12  $\mu\text{s}$ . What is the slow rate?

Sol

$$s = \frac{dV_o}{dt} = \frac{8\text{V}}{12\mu\text{s}} = 1.5 \text{ V/}\mu\text{s}$$

⑤ An opamp amplifier of gain 10 is used to amplify a sinusoidal sig with a peak amplitude of 0.5V and freq of 25 kHz. What should be the slow rate of the opamp?

Sol

$$V_i(t) = V_m \sin(2\pi f t)$$

$$V_o(t) = A_v V_m \sin(2\pi f t)$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = A_v V_m 2\pi f \cos(2\pi f t)$$

$$s = \left. \frac{dV_o}{dt} \right|_{\max} = 10 \times 0.5 \times 2 \times \pi \times 25 \times 10^3 \times 1 = 785398.16 \text{ V/s}$$

$$= 785.398 \text{ V/s}$$

### Virtual Short:

According to virtual short concept the potential difference b/w 2 i/p terminal of an opamp is almost 0 or both the i/p terminals will be at same potential i.e.  $V_d = V_1 - V_2 = 0$

$$V_1 - V_2 = 0$$

$$\boxed{V_1 = V_2}$$

Assumes that opamp is ideal. So  $R_i = \infty$

Hence  $I = \frac{V}{R} \rightarrow I_1 = I_2 = 0$

Thus voltage drop across  $R_i$  ( $V_d = IR$ ) will be 0  
So both the i/p terminal will be at same potential




### Virtual ground

If non-inverting (+) terminal of opamp is connected to ground then due to virtual short existing b/w the 2 i/p terminal, the inverting (-) terminal will also be at ground potential. Hence it is said to "virtual ground"
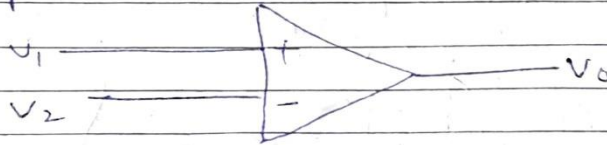
### Open and closed loop opamp


→ When there is no feedback in opamp then it is called open loop opamp




→ When there is some feedback in opamp then it is called closed loop opamp.

~~Feedback~~ (When some part of o/p is added to the i/p then it is called feedback)

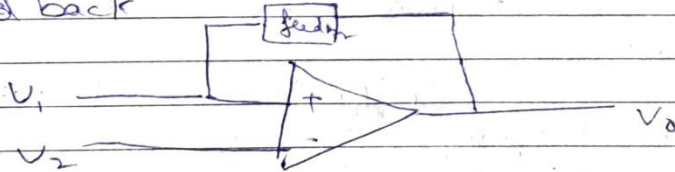→ When we give feedback at inverting terminal then it called +ve feedback



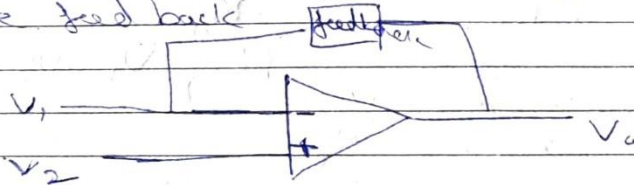
→ When we give feedback at non-inverting terminal then it called -ve feedback








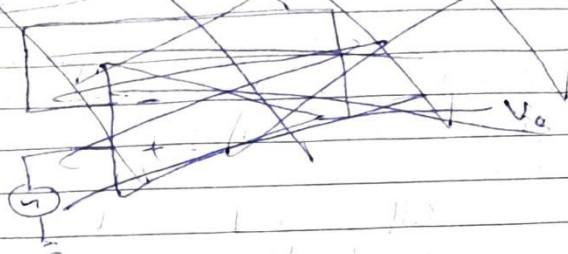~~Voltage follower (unit-gain) amplifier~~



Inverting amplifier

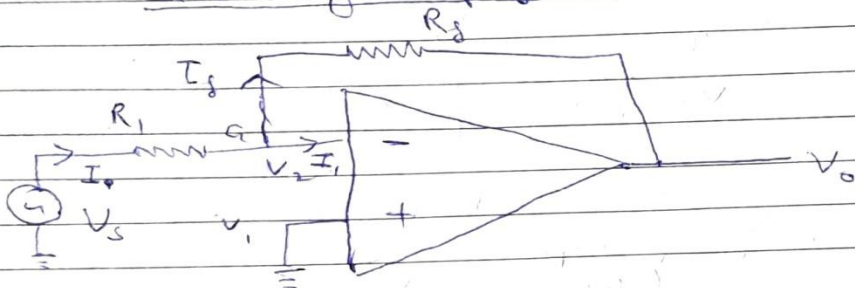

The sig which is to be amplified is applied to the inverting terminal of op-amp

Applying KCL at junction -1

we get-

$$I = I_1 + I_f$$

For ideal opamp  $I_1 = 0$

So  $I = I_f$

$$\text{or } \frac{V_s - V_2}{R_1} = \frac{V_2 - V_o}{R_f} \quad \text{--- (1)}$$

by virtual ground concept  $V_1 = V_2 = 0$


$$\frac{V_s}{R_1} = -\frac{V_o}{R_f}$$

$$-\frac{R_f}{R_1} = \frac{V_o}{V_s}$$

$$A_{vf} = -\frac{R_f}{R_1}$$



Non inverting amplifier

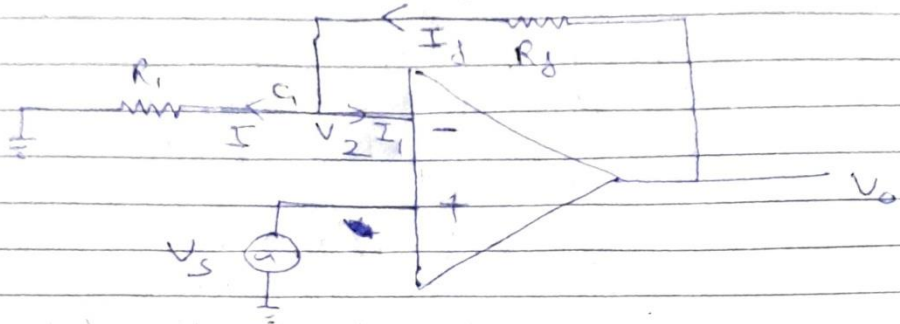

The S/g which is to be amplified is applied to the non-inverting terminal of op amp

Applying KCL at node  $a$

$$I_g = I + I_d$$

For ideal opamp  $I_1 = 0$

$$I_g = I$$

$$\frac{V_o - V_2}{R_f} = \frac{V_2 - 0}{R_i}$$

By virtual ground concept  $V_s = V_2$

$$\frac{V_o - V_s}{R_f} = \frac{V_s}{R_i}$$

$$\frac{V_o}{R_f} = \frac{V_s}{R_f} + \frac{V_s}{R_i}$$


$$\frac{V_o}{R_f} = \frac{V_s}{R_i} + \frac{V_s}{R_f}$$

$$V_o = R_f V_s \left( \frac{1}{R_i} + \frac{1}{R_f} \right)$$

$$A_{v_f} = \frac{V_o}{V_s} = 1 + \frac{R_f}{R_i}$$



Unity gain amplifier (Voltage follower)

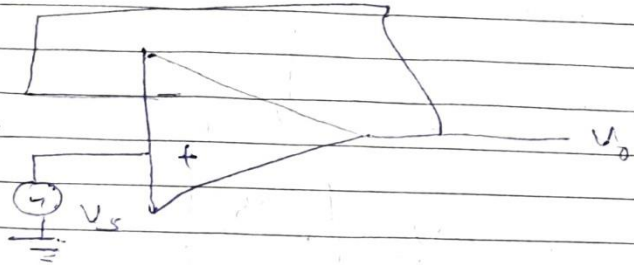

In non-inverting amplifier  $R_1 = \infty$   $R_f = \infty$

$$\text{So } A_{Vf} = 1 + \frac{R_f}{R_1}$$


$$= 1 + \frac{\infty}{\infty}$$

$$A_{Vf} = 1$$

or

$$V_o = V_s$$

Summing Amplifier (adder opamp)

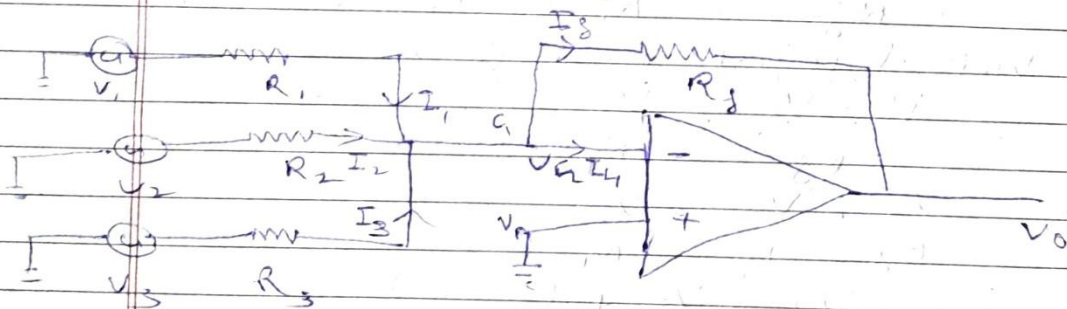

An adder is a circuit which adds all the i/p s/g to produce their addition at the o/p  
applying KCL at node a

$$I_1 + I_2 + I_3 = I_4 + I_5$$

For ideal opamp  $I_4 = 0$

$$\text{So } I_1 + I_2 + I_3 = I_5$$

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3} = \frac{V_2 - V_o}{R_1}$$





By virtual ground  $V_A = V_B = 0$


$$\text{So } \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = - \frac{V_0}{R_f}$$

$$V_0 = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

If  $R_1 = R_2 = R_3 = R_f$

$$V_0 = -(V_1 + V_2 + V_3)$$

### Integrator opamp ckt

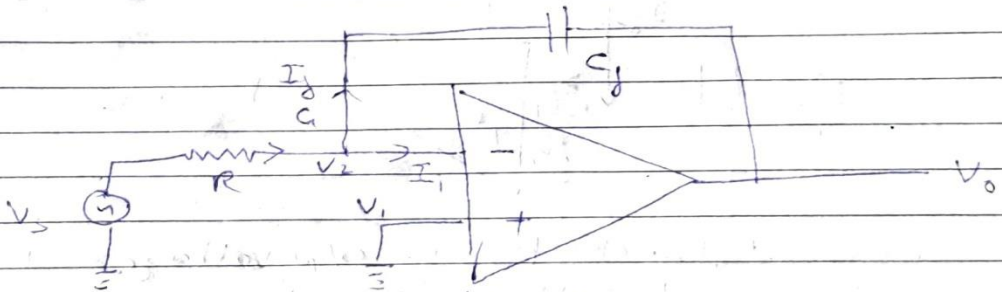

Integrator

The circuit diagram of opamp as shown in fig. Integrator ckt produces the o/p voltage which is time integral of i/p voltage.

Applying KCL at node G

$$I = I_1 + I_f$$

But for ideal opamp  $I_1 = 0$

$$I = I_f$$

$$\frac{V_s - V_2}{R} = \frac{d}{dt} (C_f V)$$

$$= C_f \frac{dV}{dt}$$

$$= C_f \frac{d(V_2 - V_0)}{dt}$$

By virtual ground  $V_2 = 0$

$$\frac{V_s}{R} = C_f \frac{d(-V_0)}{dt}$$




$$\frac{dv_o}{dt} = -\frac{1}{RC} V_s$$

Integration both side

$$\int_0^t \frac{d}{dt} v_o dt = -\frac{1}{RC} \int_0^t V_s dt$$

$$v_o = -\frac{1}{RC} \int_0^t V_s dt$$

### Differentiation opamp

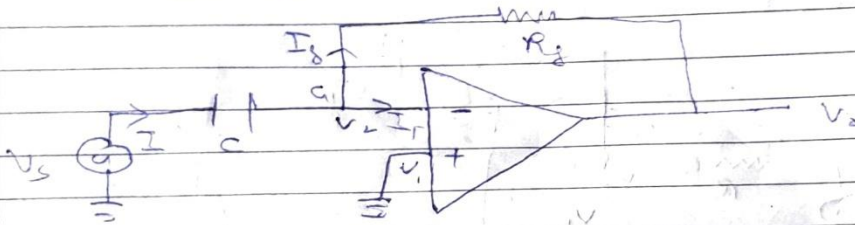

Differentiator circuit produces o/p voltage which is proportional to the time derivative of i/p voltage

Applying KCL at input node

$$I = I_f + I_i$$

But for ideal opamp  $I_i = 0$

$$I = I_f$$


$$\frac{d}{dt} CV = I_f$$

$$C \frac{d}{dt} (V_s - V_o) = -\frac{V_o - V_o}{R_f}$$

But  $V_o = 0$

$$C \frac{d}{dt} V_s = -\frac{V_o}{R_f}$$


$$V_o = -R_f C \frac{d}{dt} V_s$$

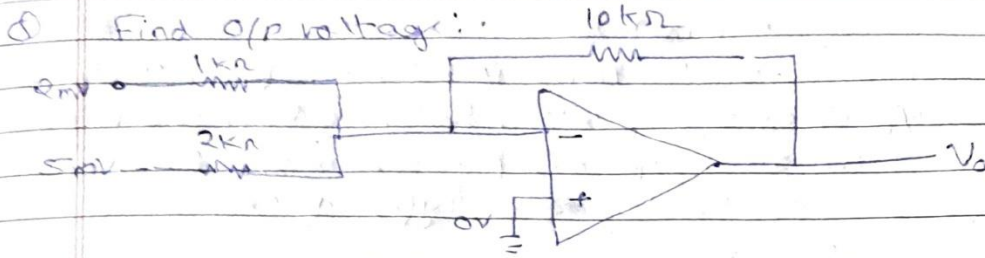

$$V_o = \left( \frac{10k \times 2mV}{1k} + \frac{10k \times 5mV}{2k} \right)$$

$$= -(20m + 25m) V$$

$$V_o = -45mV$$

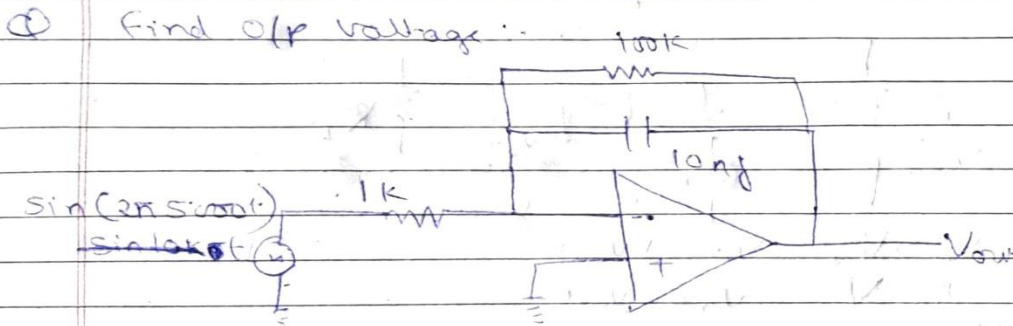

$$V_{out} = -\frac{1}{R_f} \int v_{in}(t) dt$$

$$= \frac{1}{1k \times 10n} \int \sin(2\pi 5000t) dt$$

$$= \frac{10^5}{2\pi 5000} \cos(2\pi 5000t)$$

$$= 3.18 \cos(2\pi 5000t)$$





Comparator


A comparator as its name implies compares a s/g with on one i/p of an opamp with a known voltage, called reference voltage on the other i/p and produces an o/p based on the comparison.

Types of Comparator

- ① Inverting Comparator
- ② Non-inverting Comparator


Non inverting comparator

(a). with +ve reference voltage

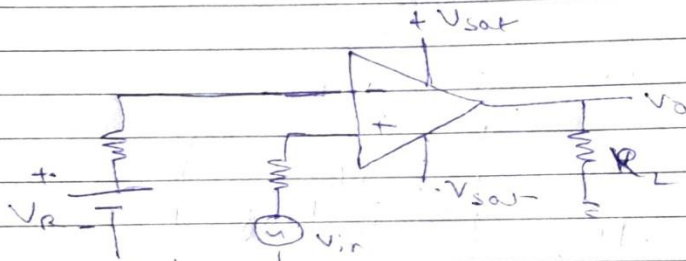

If  $V_{in} > V_r$   $V_o = +V_{sat}$   
 If  $V_{in} < V_r$   $V_o = -V_{sat}$

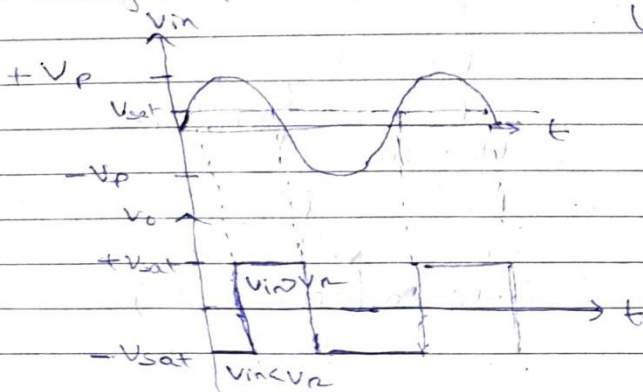Thus  $V_o$  changes b/w  $+V_{sat}$  and  $-V_{sat}$




Let  $V_{sat} = 2V$   
 $V_{in} = 5V$

(b) with -ve reference voltage




PAGE No 15-  
DATE: / / 202

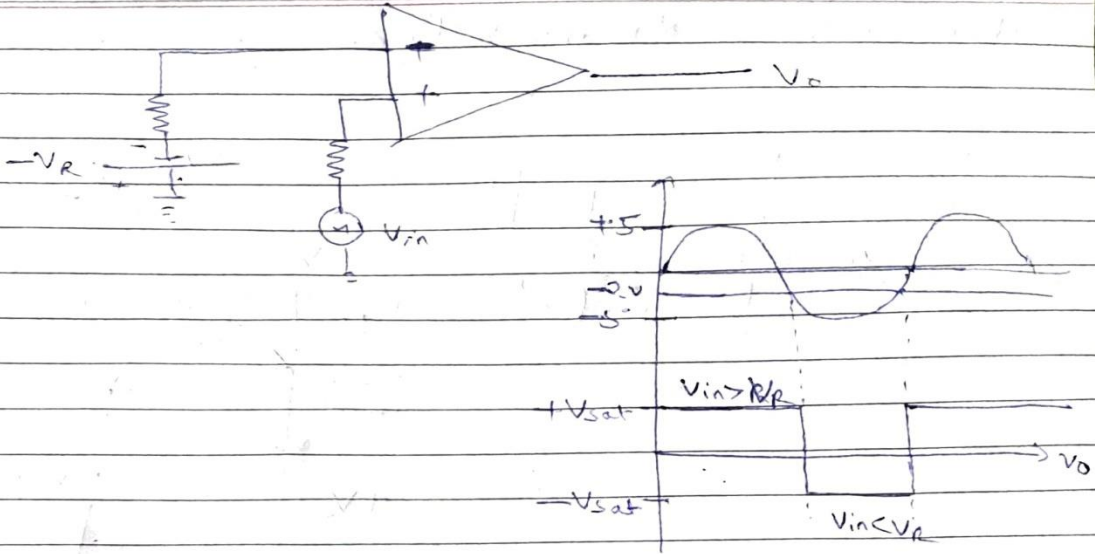

Integrating Comparator


(a) with the Reference Voltage

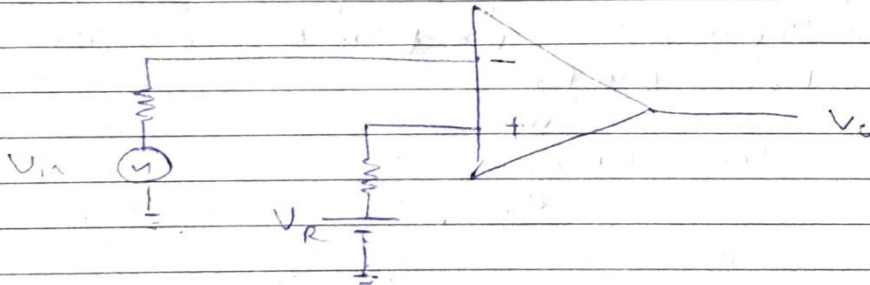

If  $V_{in} > V_R$  then  $V_o = -V_{sat}$



$V_{in} < V_R$  then  $V_o = +V_{sat}$

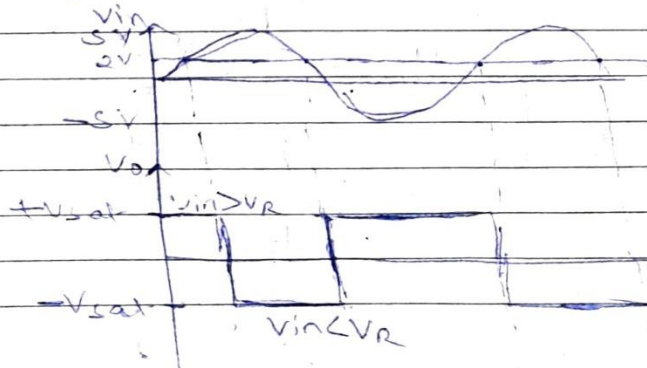Thus  $V_o$  changes b/w  $+V_{sat}$  and  $-V_{sat}$  Let  $V_{sat} = 2V$   
 $V_{in} = 5V$





(b) with -ve Reference voltage:-

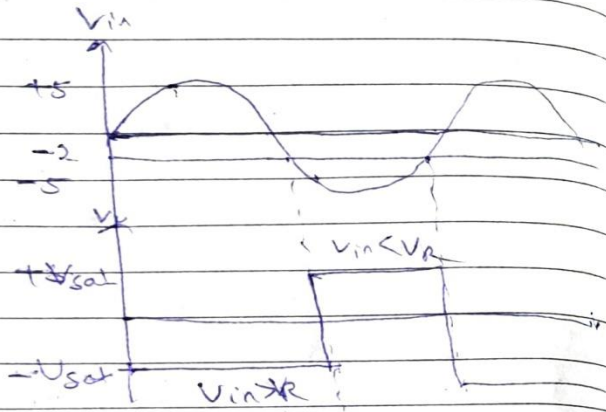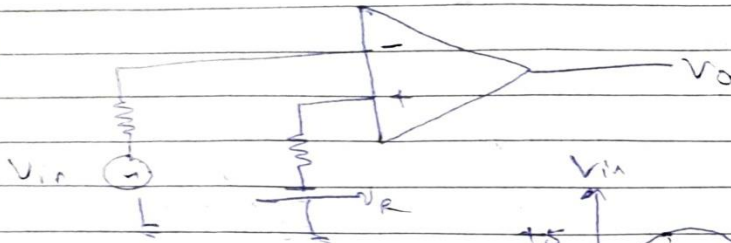

Q Design a non-inverting amplifier ckt that is capable of providing a voltage gain of 10. Assume an ideal opamp.

Sol


$$A_{v_f} = 1 + \frac{R_f}{R_i}$$

$$10 = 1 + \frac{R_f}{R_i}$$

$$\frac{R_f}{R_i} = 10$$

$$R_f = 10 R_i$$

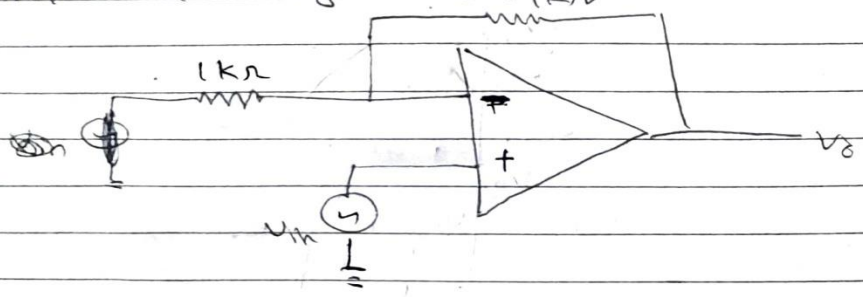Let  $R_i = 1 \text{ k}\Omega$        $R_f = 10 \text{ k}\Omega$        $9 \text{ k}\Omega$







PAGE No. 17  
DATE / / 202

Q In an opamp used as differentiator  $R = 1\text{M}\Omega$  and  $C = 1\mu\text{F}$ .  
If  $V_{in} = 2 \sin 1000\pi t$  mV calculate the o/p voltage.

Sol

$$V_o = -RC \frac{d}{dt}(V_{in})$$

$$= -10^6 \times 10^{-6} \frac{d}{dt}(2 \sin 1000\pi t) \text{ mV}$$

$$= -6.28 \cos(1000\pi t) \text{ mV}$$

Q Design an adder circuit using an opamp to get the o/p expression as under  $V_o = -(V_1 + 10V_2 + 100V_3)$ . It is given that  $R_f = 100\text{K}\Omega$

Sol

$$V_o = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] = - \left[ \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

and  $V_o = -(V_1 + 10V_2 + 100V_3)$   $\rightarrow$  ②  
Compare eq ① and ②

$$\frac{R_f}{R_1} = 1, \quad \frac{R_f}{R_2} = 10, \quad \frac{R_f}{R_3} = 100$$

$$R_1 = R_f = 100\text{K}\Omega, \quad R_2 = \frac{R_f}{10} = 10\text{K}\Omega, \quad R_3 = \frac{R_f}{100} = 1\text{K}\Omega$$

